

**LOW-FREQUENCY AMPLIFIERS  
FOR SOUND AND  
TELEVISION RECEIVERS**

15FR-2

**NATIONAL RADIO INSTITUTE**

ESTABLISHED 1914

**WASHINGTON, D. C.**



# STUDY SCHEDULE NO. 15

For each study step, read the assigned pages first at your usual speed. Reread slowly one or more times. Finish with one quick reading to fix the important facts firmly in your mind, then answer the Lesson Questions for that step. Study each other step in this same way.

1. Low-Frequency Voltage Amplification . . . . .Pages 1-8

The low-frequency amplifier consists of a voltage amplifier and an output stage. In this section you learn about the most popular voltage amplifier—the R-C coupled type—and learn how the fidelity of signal reproduction depends on parts values. Answer Lesson Questions 1 and 2.

2. More About Voltage Amplifiers . . . . .Pages 8-13

Amplitude distortion; how stages are cascaded; and the fidelity of transformer-coupled and impedance-coupled voltage amplifiers, are the important subjects of this section. Answer Lesson Questions 3 and 4.

3. Single-ended Power Amplifiers . . . . .Pages 13-19

Loudspeakers require signals with considerable power. Therefore, in sound receivers, the voltage amplifier supplies signal voltage to the grid of a power output tube. This section describes the differences between voltage amplifier and power stages. Answer Lesson Questions 5 and 6.

4. Push-Pull Power Stages . . . . .Pages 19-25

The push-pull output connection offers higher power and better fidelity than does a single-ended power stage. Study this section carefully; there is much to learn about this important circuit. Answer Lesson Question 7.

5. Inverse Feedback . . . . .Pages 25-30

Much of the distortion that arises in pentode and beam power output tubes can be eliminated by feeding back an out-of-phase signal so as to cancel some of the distortion. Here you learn how inverse feedback circuits of this kind work. Answer Lesson Question 8.

6. Phase Inverters . . . . .Pages 31-34

Phase inverters are tube stages used in place of the input push-pull transformer. These stages reverse the signal phase  $180^\circ$  so that the push-pull grids may be properly driven. Answer Lesson Questions 9 and 10.

7. Facts about Low-Frequency Amplifiers . . . . .Pages 34-36

This is a review section for the lesson. If you do not understand all of it, you should review the proper sections. Later on, this summary will help to refresh your mind on the basic characteristics of low-frequency amplifiers.

8. Mail your Answers for this Lesson to NRI for Grading.

9. Start Studying the Next Lesson.

# LOW-FREQUENCY AMPLIFIERS FOR SOUND AND TELEVISION RECEIVERS

## Low-Frequency Voltage Amplification

**R**ADIO signals go through several receiver sections to reach the low-frequency amplifier. As a review, you will recall that the signals (picked up by the receiving antenna) consist of radio frequency variations that follow the speech, picture, code, or music intelligence. The desired modulated carrier is selected and amplified by the r.f. and i.f. amplifiers. Next, the signal is fed into the demodulator (also called the detector). The demodulator stage eliminates the carrier, and produces a signal that is the electrical equivalent of the original intelligence—the signal can now be used to reproduce the sounds or picture we want, except that it is too weak to operate the reproducer. The job of the low-frequency amplifier is to increase the voltage or the power of this signal (from the demodulator) sufficiently to operate the reproducer.

**Requirements.** An increase in the signal voltage is all that is required to modulate the electron stream in the image reconstructor tube of a television set. However, the loudspeaker of a sound receiver may require considerable *power*—it is common to find sound receivers with power outputs ranging from 1 watt to as high as 10 or 12 watts. (Public address systems range up to 100 watts and more.)

By proper design, it is possible to obtain the necessary power from one or more "power" tubes, provided sufficient signal voltage can be applied to the control grid of this tube (or tubes). To obtain this signal voltage, the output of the demodulator is fed through

one or more *voltage* amplifier stages. These voltage amplifier stages plus the power output stage make up the complete low-frequency amplifier. (The cathode ray tube or picture reproducer is the output stage in a television receiver.)

Since the low-frequency amplifier deals with the electrical equivalent of the original intelligence, the amplifier must of course create as little distortion as possible. Amplitude and frequency distortion must be controlled in a sound receiver, and in a television set the designer must worry about phase distortion, also.\*

► In this lesson, we shall study the complete low-frequency amplifier. (Future lessons will cover r.f. and i.f. amplifiers and demodulators.) We will begin with voltage amplifiers and then go into power stages.

We find that low-frequency *voltage* amplifiers are classified according to the devices used to couple the stages together. Thus, we have the resistance-capacitance coupled amplifier, the impedance-coupled amplifier, and the transformer-coupled amplifier. Of these the resistance-capacitance type (commonly known as the "resistance-coupled" or as the "R-C" amplifier) is the most widely used, so we will start with it.

---

\*The low-frequency amplifier in a sound receiver is called the *audio amplifier* (because it handles frequencies corresponding to the audible range), and that in a television receiver is called the *video amplifier*.

## THE R-C AMPLIFIER.

Fig. 1 shows the details of resistance-capacitance coupling, so named because resistors and condensers serve to couple one tube to another.

You have met the amplifier before, but let's study its operation in more detail. As you have learned, the filaments are supplied with heater power, even though it is customary not to show the filament connections on schematic diagrams of the kind shown in Fig. 1. (This is purely a convenience to avoid complicating the diagram when it is being used to study the signal paths.) The plate supply is indicated by the signs  $B+$  and  $B-$ . Grid bias is obtained from the self-bias resistors  $R_2$  (for  $VT_1$ ) and  $R_5$  (for  $VT_2$ ). The a.c. components of the plate currents are by-passed around these resistors by  $C_2$  and  $C_5$  respectively. That is, there is only a small a.c. voltage drop between the tube cathodes and  $B-$ , because the reactances of the condensers are lower than the resistances of the resistors they by-pass. However, the d.c. current has to flow through the bias resistors, and the resistor values are chosen so that they provide the voltage drop needed to furnish the desired grid bias.

► The input signal voltage  $e$  causes a signal current to flow through  $C_1$  and  $R_1$ . The resulting voltage drop across grid resistor  $R_1$  becomes the grid signal voltage for  $VT_1$ . (The signal current is a.c., so it "passes through" the condenser. Hence, the entire a.c. voltage  $e$  appears across  $R_1$  except for the portion lost in the reactance of the condenser, as we shall soon show.) Tube  $VT_1$  amplifies the signal, so an amplified version appears across plate load resistor  $R_3$ . This load a.c. voltage causes a signal current to pass through condensers  $C_3$  and  $C_4$ , and grid resistor  $R_4$ . The resulting voltage across  $R_4$

becomes input for  $VT_2$ .

Condenser  $C_3$  is called the *coupling condenser* because it "couples" the circuits of  $VT_1$  to those of  $VT_2$ . Condenser  $C_4$  also could be considered as a coupling condenser, but instead it is called a by-pass condenser, because it is primarily selected to by-pass the signal so that the signal current does not flow through the B supply. (This condenser completes the a.c. circuit to ground, so that the signal is directly applied to the grounded end of resistor  $R_4$ .) This completes the passage of the signal through the stage using  $VT_1$ ; it now is acted upon by  $VT_2$ .

**Frequency Band.** Before we can determine the gain of the stage using tube  $VT_1$ , we must consider the range or "band" of frequencies that this amplifier is called upon to pass.

The use to which the receiver is put determines the width of the band of frequencies that the low-frequency amplifier must pass. Communications receivers, intended only for the reception of voice or code signals, have to amplify only those frequencies between about 200 and 3000 cycles.\*

Sound receivers for the home must amplify a wider band for musical reproduction. Although sound frequencies range from 30 cycles to above 16,000 cycles, the average inexpensive radio is limited to a frequency range of from about 200 cycles to 5000 or 6000 cycles. Some of the better receivers, including the average f.m. receiver, have ranges of 50 cycles to 8000 cycles. A few high-fidelity a.m. and f.m. receivers have a range of from 30 to 16,000 cycles.

In television, the desired frequency band ranges from 10 cycles to near 4,000,000 cycles. This band is so wide

---

\*Like most radio men, we use "cycles" for "cycles per second," which is the correct term.

that special compensators are necessary, as we shall soon see.

► Even though the low-frequency amplifier is intended to pass a particular band of frequencies (as we just described), the amount that it amplifies the higher and lower frequencies in this band is different from the amplification given to frequencies in the middle of the band. That is, it is not perfect in its frequency response, and it may not be economical to improve the response beyond a predetermined level. Therefore, the parts are chosen to give a certain response, and this places limits on the replacement values that

come from changes in the load, or from voltage-dividing networks that vary with frequency. Let's see what occurs in our R-C amplifier of Fig. 1.

**Mid-Frequency Response.** First, let's consider the response to frequencies in the middle of the band. If the amplifier is designed to pass (reasonably well) frequencies between 100 cycles and 5000 cycles, then we can call frequencies from 1000 to 3000 cycles the mid frequencies.

When we examine the parts values used in an R-C amplifier in an a.m. or f.m. receiver, we find that the capacity used as  $C_4$  in Fig. 1 is always so large

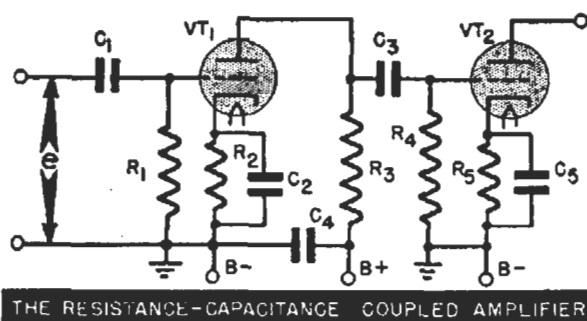


FIG. 1. This R-C coupled amplifier is the basic circuit found in most sound and television low-frequency amplifiers.

can be used. Hence, it is advisable to learn more about how an R-C amplifier (as found in a.m. and f.m. receivers) responds to the middle, low, and high frequencies in its pass band.

### FREQUENCY RESPONSE

You know that the gain of a stage depends on the amplification factor ( $\mu$ ) of the tube, the tube's plate resistance, and the value of the load impedance. The grid voltage is stepped up by the factor  $\mu$ , and the resulting equivalent a.c. plate voltage ( $\mu e_g$ ) is then divided between the plate resistance and the load. Therefore, since  $\mu$  and the plate resistance remain the same almost regardless of frequency, any change in the over-all gain must

that this condenser has negligible reactance to *all* frequencies in the band to be passed. Also,  $C_3$  has little opposition to the mid frequencies, so there is practically no reactance between  $R_3$  and  $R_4$  at these mid frequencies. Therefore, *insofar as a mid-frequency signal is concerned,  $R_4$  is connected in parallel with  $R_3$  and the combination forms the load for  $VT_1$ .* Thus, the equivalent circuit at the mid frequencies is as shown in Fig. 2A.

You will recall that the higher the load resistance is made, the greater the voltage gain will be. In fact, we get almost 90% of the  $\mu$  of the tube as a stage gain when the load resistance is 10 times the a.c. plate resistance  $r_p$ . So you might think that we need only to increase the values of  $R_3$  and  $R_4$  in or-

der to get more gain. That is true, but there are practical limits on the values we can use—we will take these up after we see what happens at the low and high frequencies.

**Low-Frequency Response.** When we go down to low frequencies (those lower than the mid frequencies) we find that the coupling condenser ( $C_3$  in Fig. 1) comes back into the picture, because, as the frequency decreases, the condenser reactance increases. Hence, it begins to act with  $R_4$  as a voltage divider. In other words, as shown by the equivalent circuit of Fig. 2B, the signal voltage developed across plate resistor  $R_3$  is actually fed into a filter  $C_3$ - $R_4$ , which passes higher frequencies better than lower frequencies. As the frequency decreases, the reactance of  $C_3$  increases; a greater proportion of the signal voltage is then dropped across  $C_3$ , and less appears across  $R_4$ . Since  $VT_2$  is operated *only* by the signal voltage across its grid resistor  $R_4$ , the less this voltage is, the lower the  $VT_2$  input signal will be. Therefore, there is less voltage fed to  $VT_2$ , so the over-all grid-to-grid ( $VT_1$  to  $VT_2$ ) gain is less, and the gain drops still more as the frequency is decreased further. Hence, in the low-frequency range, this circuit has frequency distortion (unequal amplification of different frequencies).

**High-Frequency Response.** The equivalent circuit for high frequencies is given in Fig. 2C. Condenser  $C_3$  is no bother because its reactance at high frequencies is negligible. However, we now have a new factor, the capacity  $C_s$ , which represents a number of different tube and stray circuit capacities that we have lumped together for convenience. These capacities do not appear in Fig. 1 (we will explain them shortly), but you can see their result at once. Since the reactance of  $C_s$  de-

creases as frequency is increased, it will act as a shunt across the resistors at higher frequencies. In effect, this reduces the load value at higher frequencies, so more and more of the signal voltage will be lost across  $r_p$  within tube  $VT_1$ . Hence we have frequency distortion at the higher frequencies also, but from another cause.

► We have given the three equivalent circuits together in one drawing so that you can compare them with each other. Notice that the schematic (Fig. 1) shows the electrical connections, *but does not directly indicate how the circuit will act at different frequencies.* Even the equivalent circuits of Fig. 2 indicate only the trend of operation; until parts values are known we cannot tell how serious the frequency distortion may be. As we will now show, *changing the parts values will radically change the response.*

## EFFECT OF PARTS VALUES

We can continue to assume that  $C_4$  in Fig. 1 is sufficiently high in capacity to have no effect on any frequencies the amplifier is designed to pass. Therefore, we can concentrate on the limits set for the parts  $R_3$ ,  $R_4$ ,  $C_3$ , and  $C_s$  of Figs. 1 and 2.

**Value of  $R_3$ .** The value of the load is one of the factors that determine the stage gain. Since we want the stage to amplify, you might imagine that the value of plate resistor  $R_3$  should be high. It is desirable to have this a high resistance at the middle and low frequencies, but not at the higher frequencies. This is because the higher the resistive load is, the sooner  $C_s$  becomes an effective shunt. This effect is shown by Fig. 3. Here, curve A shows the frequency response for a high load resistance, and curve B the response for a much lower load resistance (assuming the same value of  $C_s$  in each case).

Naturally, the higher the load resistance is, the higher the amplification at the mid frequencies. Therefore, curve A shows fairly high gain at around 2000 cycles—higher than that shown by curve B.

However, compare the output at 2000 cycles with that at 5000 cycles for

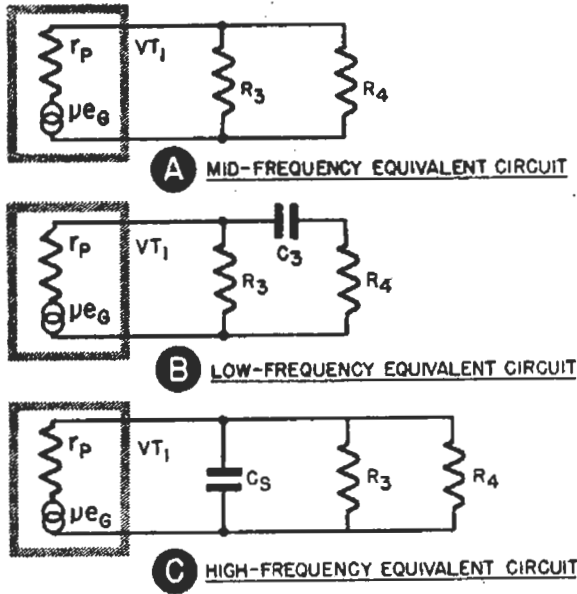


FIG. 2. The R-C amplifier responds differently to the high, middle, and low frequencies in its pass band. These equivalent circuits show how the circuit components affect the response.

curve A. There is a severe loss of higher frequencies (frequency distortion) beginning at about 4000 cycles. On the other hand, curve B shows a much smaller difference between the mid-frequency response and that at 5000 cycles. In other words, the gain shown by curve B drops only from 5 to about 3 in the range from 2000 to 5000 cycles, whereas the gain shown by curve A changes from 10 to about 3 over the same frequency range.

The ideal amplifier—one having no frequency distortion—would amplify all frequencies in its pass band equally. Hence, curve B approaches the ideal more closely than does curve A. This shows that there is good reason for keeping the effective load for the stage low when high fidelity is desired. (However, this reduces gain, and often

a compromise is necessary to get reasonable gain with good fidelity.)

► In addition, the d.c. plate current of  $VT_1$  passes through  $R_3$ , and this brings up a power supply problem. The drop in  $R_3$  (caused by the d.c. plate current) is subtracted from the B supply voltage. The remainder is the plate-cathode voltage actually supplied to the tube, and we want this voltage to be reasonably high. Since there are limits to the power supply voltage, the value of  $R_3$  must be kept down to avoid too much d.c. voltage drop. The most common values in a.m. and f.m. home receivers range from 50,000 ohms to 250,000 ohms. Therefore, the gain of a practical R-C amplifier stage is not as high as is theoretically obtainable.

**Value of  $R_4$ .** Increasing the resistance of  $R_4$  seems to be another way of

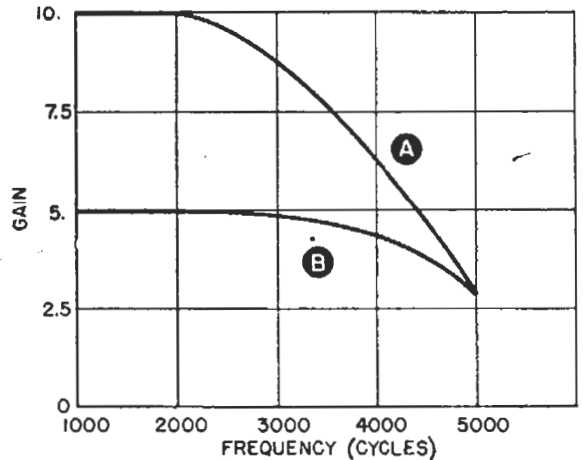


FIG. 3. Using a higher load value gives greater gain (curve A), but there is a more rapid drop-off in the high-frequency response.

getting a higher load value, since this resistor is in parallel with  $R_3$ , and in addition, no d.c. is supposed to flow through it. However, if the following tube ( $VT_2$  in Fig. 1) is a power tube, we may encounter gas trouble.

No matter how well a tube is evacuated in manufacture, some gas (air) remains in it. The heat of operation may drive gas molecules out of the

“pores” of the metal elements. When the gas level upsets operating conditions, we say that the tube is “gassy.” This trouble occurs particularly with power tubes because of their high current levels.

When the tube becomes gassy, speeding electrons strike the gas molecules and knock out electrons, leaving positive gas ions. The positive gas ions move toward the cathode, but some “capture” electrons from the grid. This causes an external electron flow to the grid element. This electron flow must pass through  $R_4$ , and therefore, develops a voltage across it. The grid current may be quite small at first. However, if resistor  $R_4$  is very high in value, then even a very small gas current will cause an appreciable drop across it.

The voltage drop that occurs when the tube is gassy has a polarity that makes the grid end of  $R_4$  positive. Hence, the drop opposes the bias voltage, and causes a reduction of the grid bias. Consequently, there is an increase in plate current. Eventually, the higher than normal plate current, and the bombardment of the cathode by the heavy gas ions will destroy the emissive properties of the cathode and thus ruin the tube.

For this reason, there is a definite upper limit to the size  $R_4$  can have. If tube  $VT_2$  is a power tube,  $R_4$  must be no more than 100,000 ohms to 250,000 ohms in most cases.

If the tube is not a power tube, there is less gas trouble, and  $R_4$  can be larger in value. You may find voltage amplifiers using values from 250,000 ohms to as high as 10 megohms.

**Value of  $C_3$ .** The value of  $C_3$  needed for good low-frequency response depends on the value of  $R_4$ . If  $R_4$  can be a high resistance, then even a small capacity can be used without

excessive loss of the low frequencies. However, we have just shown that  $R_4$  cannot always be made so large; therefore,  $C_3$  may have to be fairly high in capacity.

► The low-frequency response of a radio receiver depends on the design of a number of things—the large amount of audio power needed for good low-frequency response requires an oversized loudspeaker, a large power supply, a high-power output stage, and a large console with a specially designed speaker compartment. All these items are costly, a fact that explains why the low-frequency response is sacrificed in the average receiver.

Once the limits have been set by the design of these components, there is no reason for making the voltage amplifier too perfect in its response; in fact, it is better *not* to have the low-frequency response too good, because if the amplifier can amplify very low frequencies, slight changes in the power supply voltages may cause it to oscillate. This oscillation prevents the passage of the signal, so all that can be heard is either a low-frequency howl or a “putt-putt-putt” sound called *motorboating*. Therefore,  $C_3$  and  $C_1$  of Fig. 1 are made no larger than necessary in practical amplifiers. Values found in the average radio are from .005 mfd. to perhaps .1 mfd., with the most common values being .01 or .05 mfd.

**Value of  $C_s$ .** The shunt capacity  $C_s$  is made up of the inter-electrode capacities within the tubes, and the capacities between wires and parts in the circuit.

The tube inter-electrode capacities are shown for a triode tube in Fig. 4. You will recall that a capacity exists between any two conductors separated by an insulator. Therefore, the metallic tube elements, separated by a vacuum,



form tiny condensers. As shown by Fig. 5, the capacity between the grid and the cathode (called  $C_{GK}$ ) is across the input circuit, and the capacity between the plate and the cathode (called  $C_{PK}$ ) is across the output circuit. Even worse is the capacity between the grid and the plate ( $C_{GP}$ ). Notice that this capacity acts as a coupling condenser between  $R_L$  and the input, so that part of any a.c. voltage across  $R_L$  will also be across the input. This means that part of the amplified signal voltage across the load will feed back to the input circuit through  $C_{GP}$ . Because of the phase relationships involved, the reaction of this feedback voltage on the input is such that the circuit acts as if the input capacity of the tube were far higher than the measured capacity between the grid and the cathode elements.

► Therefore, going back to Fig. 1, tube  $VT_2$  acts as if it had a high capacity between its grid and its cathode, in parallel with  $R_4$ . Also, tube  $VT_1$  has an output capacity between its plate and

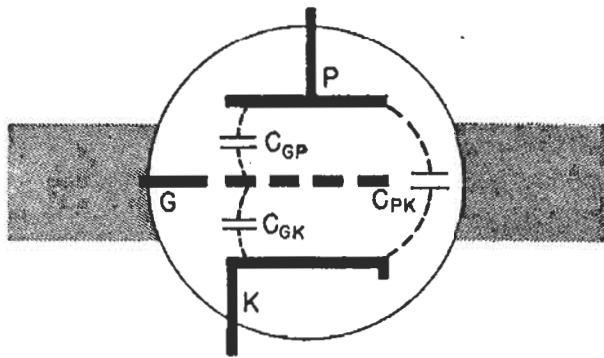


FIG. 4. The inter-electrode capacities within a triode tube.

its cathode (across  $R_3$ ), and there is stray capacity between the chassis and the wiring and parts. (Coupling condenser  $C_3$  is the most bulky part, so a considerable amount of stray capacity exists between it and the chassis. This is another reason for choosing  $C_3$  with a capacity that is no larger than necessary—if its physical size is kept down,

the stray capacity will likewise be minimized.)

Since the output capacity of  $VT_1$  and the input capacity of  $VT_2$  are in parallel, they can be lumped together and considered as a single condenser. Therefore, at high frequencies, the circuit is equivalent to that shown in Fig. 2C, where capacity  $C_s$  represents all the shunting capacities.

► Set designers make every effort to minimize the value of  $C_s$ . Once this

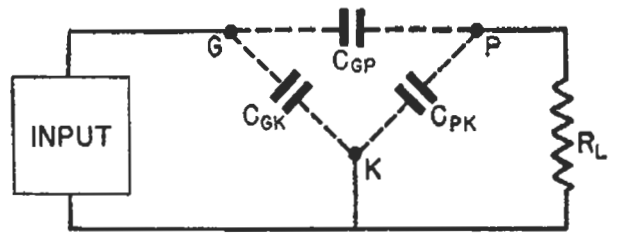


FIG. 5. The plate-grid inter-electrode capacity provides a coupling path so that the voltage across the load is transferred to the input circuit.

value is determined, it fixes the largest values of  $R_3$  and  $R_4$  that can be used and still have the required fidelity.

**Summary.** Tube  $VT_1$  is usually chosen to be a high- $\mu$  triode (or pentode in some cases). Tubes with high gain and low d.c. current values have been specially designed for use in R-C amplifiers. Even so, fidelity compromises mean that R-C amplifiers are used where gain is less important than fidelity, because it is possible to get good fidelity, despite what has just been shown, if the gain can be sacrificed. Hence, we can make the following rules for circuits like that in Fig. 1:

1. For maximum gain at the middle and low frequencies,  $R_3$  and  $R_4$  should be high in resistance.

2. For minimum loss of high frequencies,  $R_3$  should be low in resistance.

3. The larger  $C_3$  is in capacity, the better is the low-frequency response.

► As a serviceman, you will have to replace these parts whenever defects

occur in them. You should use replacements having values within 20% of the original values if you do not wish to change the circuit characteristics. If you do want to make a change, or if you do not know the original values, the rules just given will help you

choose the best replacements for the desired conditions. When you install replacements, take care to minimize the shunting capacity  $C_s$ . Don't add more wire than necessary, and don't disturb positions of parts more than is necessary.

---

## More About Voltage Amplifiers

So far, we have considered the frequency response and frequency distortion of a resistance-coupled amplifier. Equally important is the amplitude distortion that can occur—in fact, even small amounts of amplitude distortion can be far more objectionable than fairly large amounts of frequency distortion. Let's continue with the resistance-coupled voltage amplifier as our example, and learn more about amplitude distortion.

### AMPLITUDE DISTORTION IN R-C AMPLIFIERS

You know that amplitude distortion is produced whenever the wave shape of a signal is changed. This distortion will occur whenever the tube's operating characteristic is curved. Therefore, to minimize the distortion, operation is limited to the straightest portion of a tube's characteristic.

► However, so far we have presented the darker side of this story because we have shown you only the characteristic curve of the tube *alone*. Such "static" characteristic curves show how the tube operates when there is *no plate load*. These curves are the kind the tube manufacturer can most easily furnish since he doesn't know just what load values may be chosen by the set designer. However, when the tube is operated with a load (the normal condition) its operation is over a "dy-

namic" characteristic that is considerably different in shape. Naturally, we are interested in dynamic curves because they show how a tube actually operates in a stage.

Dynamic curves can be found by actually setting up the circuit and measuring the response, or they can be plotted from the static curves. We won't go into their construction here, but the following facts will show why they differ so much from the static curves.

First, you know that the plate current of a tube with no load increases rapidly as the grid bias is made less negative. Curve *A* of Fig. 6 is a typical static curve, showing how the plate current and the grid voltage are related when the tube plate voltage is a fixed amount.

Next, you have learned that when a load resistor is used, some of the B supply voltage is dropped across it because the tube plate current flows through this resistor. Therefore, the actual plate-cathode voltage of a tube is the difference between the d.c. load drop and the supply voltage.

► Now, let's suppose we change the bias so that the grid is made less negative. Since the plate current tends to increase when the bias is less negative, there will be a greater drop across the load resistor, so the actual tube plate voltage drops. This reduction in plate

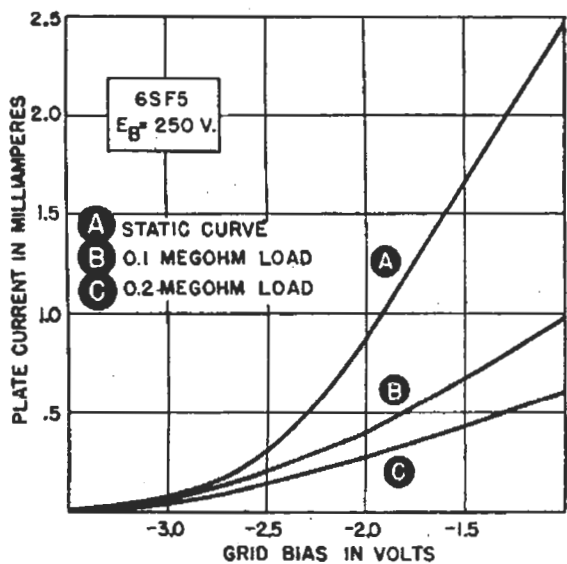


FIG. 6. Curves B and C show how increasing the load resistance tends to flatten the tube  $E_{g1}-I_p$  characteristic curve.

voltage counteracts some of the plate current change (the plate current depends on both the grid voltage and the plate voltage) so the actual change in current for a particular grid voltage change is not as large when a load is used.

Hence, when a load is used, the tube characteristic is "ironed out" so that it is much flatter and straighter than the static curve. The effect of this self-regulation is shown in Fig. 6, where curves B and C represent dynamic curves for two different load values for a triode tube.

You can see that there is far less curvature in these dynamic curves than there is in curve A. This means that there will be much less amplitude distortion when a load is used. That is, a change in grid voltage (such as is

caused by a signal) will cause much more nearly linear plate current changes.

► Furthermore, the higher the load resistance is, the flatter the curve. However, this brings back our compromise conditions; you know that high resistances cause excessive loss of the higher frequencies. Therefore, the designer must consider gain, frequency distortion, and amplitude distortion when he chooses values for the tube load.

## CASCADE AMPLIFIERS

These factors are further complicated when there is more than one stage of R-C amplification. For example, suppose we have two stages, as shown in Fig. 7. We'll consider tubes  $VT_1$  and  $VT_2$  to be the voltage amplifying tubes for these stages, with  $VT_3$  shown only to indicate the output coupling. Furthermore, let's assume that the characteristics of *corresponding* parts are alike: that is, the tubes are the same, condensers  $C_4$  and  $C_7$  have the same capacity, and resistors  $R_3$  and  $R_6$  have the same resistance, as do  $R_4$  and  $R_7$ .

The first thing we are interested in is the amount of amplification we get. Let's suppose that each of the stages is capable of giving a gain of 10 at the mid frequencies, and that a signal of 1 volt is applied to the input of  $VT_1$ . There will be a signal of 10 volts across  $R_3$ ; this voltage is applied to tube  $VT_2$ .

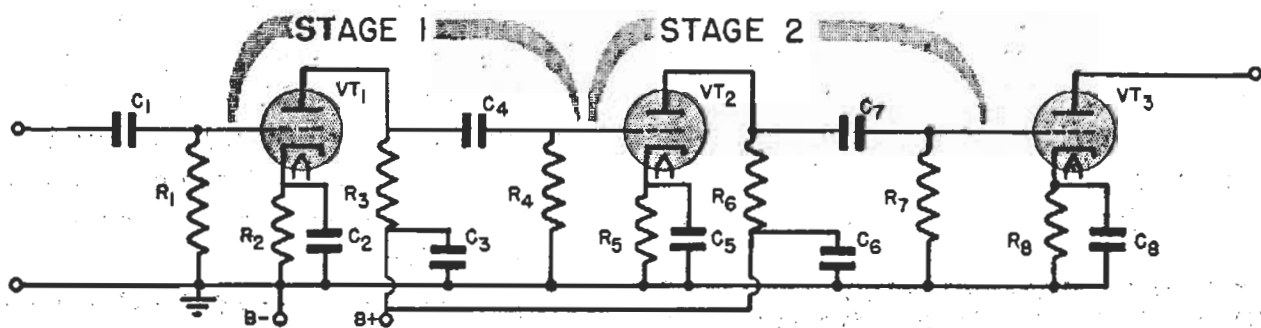


FIG. 7. A two-stage R-C amplifier.

This tube also has a gain of 10, so its 10-volt grid signal is raised to 100 volts\* across  $R_c$ . Thus, the gain of successive stages is the *product* of their respective gains; the gain of the  $VT_1$  stage is multiplied by the gain of the  $VT_2$  stage ( $10 \times 10 = 100$  and our 1-volt signal was raised to 100 volts).

When more than one stage is used, we say that the stages are "in cascade," because each one steps up the signal output of the previous ones by its own gain factor.

**Fidelity.** From this, we might at once assume that all we need to do to

with two stages it will be one-quarter (one-half times one-half) that of the mid frequencies.

► *This is one of the reasons why the number of low-frequency amplifier stages is kept at a minimum in radio receivers. It is far better to use a single high-mu triode or pentode tube than to use two or more stages of low-gain triode tubes.*

## TELEVISION AMPLIFIERS

Although careful design is necessary to have high fidelity in a resistance-

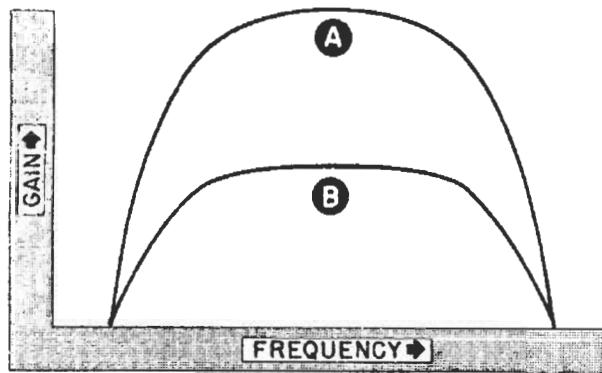


FIG. 8. Curve A shows that there is a higher mid-frequency gain when two stages are used, but there is a more rapid drop-off at the lower and higher frequencies.

obtain more gain is to add more stages. However, if we do, we find that the fidelity becomes much worse when more than a single stage is used.

For example, see Fig. 8. Curve B represents the fidelity of a single stage, and curve A represents that of two identical stages. Curve A shows that the gain is increased at the mid frequencies, but you can see that the addition of another stage exaggerates the frequency distortion already present at the low and high frequencies in one stage. Thus, if the gain at some particular frequency is only half that of the mid frequencies in a single stage,

coupled amplifier, this circuit still offers a greater range of frequency response than any other, so it is universally used (in a modified form) as the video intelligence signal amplifier in television receivers. We will leave complete details for later lessons, but some of the methods used to get a broad frequency pass band are of particular interest at this time.

For television, the frequency range is from about 10 cycles to as high as 3,000,000 or 4,000,000 cycles. This is many times greater than that found in any sound receiver. Getting this extended high-frequency response is quite a problem.

To reduce the effect of the shunting capacity (corresponding to  $C_s$  in Fig.

\*If the input was .01 volt, the output of  $VT_1$  would be .1 volt, and the output of  $VT_2$  would be 1.0 volt.

2C) and thus obtain better high-frequency response, a very small load resistor (1000 to 5000 ohms) is used. This means extremely low gain unless special high mutual-conductance pentode tubes are used.

Other steps are also taken to reduce the effects of the shunt capacity. As you learned, the shunt capacity is due

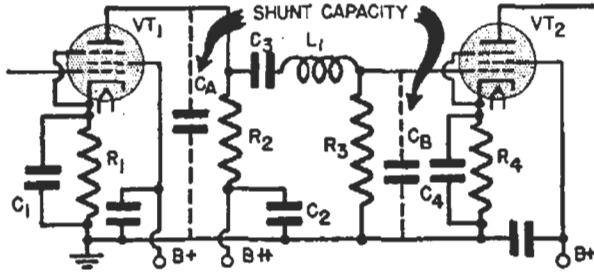


FIG. 9. The effects of the shunt capacities  $C_A$  and  $C_B$  are reduced by using  $L_1$ .

partly to the output capacity of one tube and partly to the input capacity of the other. In Fig. 9, these capacities are represented as  $C_A$  and  $C_B$ . One scheme used is to insert a coil (coil  $L_1$  in Fig. 9) between the plate circuit of  $VT_1$  and the grid circuit of  $VT_2$ . This serves to isolate  $C_B$  from  $R_2$ , so it reduces the effects of  $C_B$  on the load of  $VT_1$ . The isolation increases with frequency increases because the reactance of  $L_1$  increases with frequency. Hence, its increasing reactance counteracts the decreases of the  $C_B$  reactance insofar as  $VT_1$  is concerned.

Also it is possible to make  $L_1$  and  $C_B$  resonant at some rather high frequency. This forms a series resonant circuit so that a maximum voltage appears across  $C_B$  at the resonant frequency. This voltage is applied to  $VT_2$ , so the response at and near this resonant frequency is improved.

► Another scheme is shown in Fig. 10. Here, coil  $L_2$  is placed in series with  $R_2$ . As the frequency increases, so does the reactance of  $L_2$ . Therefore, as  $L_2$  is part of the load, the load impedance rises as the frequency increases. Al-

though the shunting effects of the stray capacity are increased, there is a better division of the  $\mu e_G$  voltage between the  $r_P$  of  $VT_1$  and the load, so the  $VT_1$  stage provides higher gain at the higher frequencies. This tends to minimize the drop-off in high-frequency response. Furthermore, by making  $L_2$  resonant with  $C_A$  (at a high frequency), a parallel resonant circuit is formed. This provides a rise in the load resistance at resonance, which in turn further boosts the gain at the high frequencies. Sometimes both schemes shown in Figs. 9 and 10 are used in the same amplifier.

► In addition to these methods of reducing shunt capacity effects, television engineers use sockets that have low capacity to chassis, and mount parts so that they are separated from the chassis as much as possible, yet try to keep the leads between stages short to avoid capacity between these leads and other wires. These precautions are necessary because of the very wide

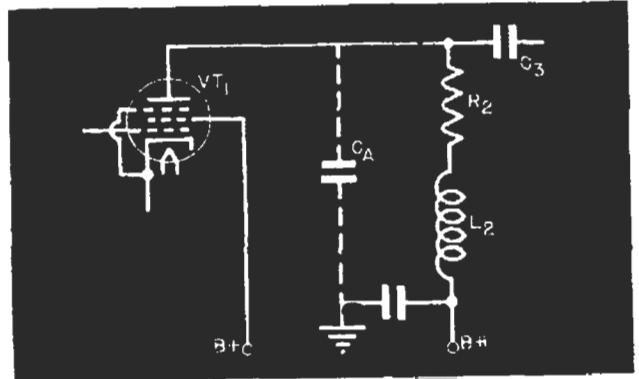


FIG. 10. Another compensation for shunt capacity is to use  $L_2$  in series with the load resistance.

band of frequencies passed by the television amplifier. Naturally, it is not necessary to go to such extremes in ordinary sound receivers.

### USING COILS FOR COUPLING

The resistance coupling you have just studied is the coupling method most commonly used today for voltage amplifiers. However, some amplifiers

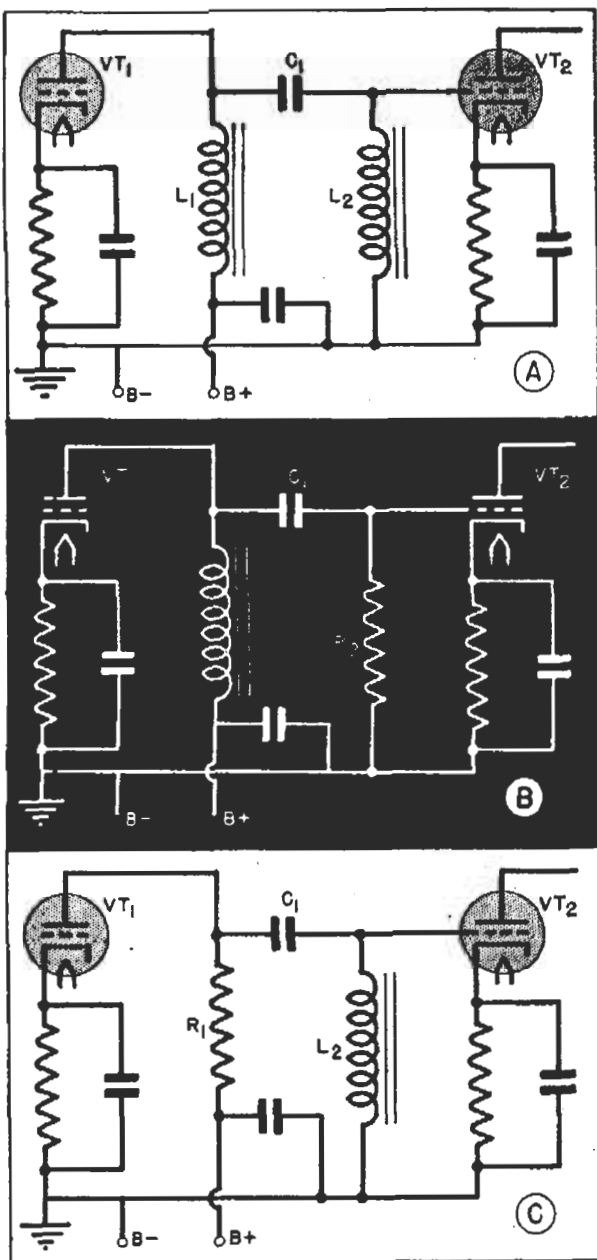


FIG. 11. Three forms of impedance coupling are used in low-frequency amplifiers.

use inductances (coils) for coupling. Some of these inductances are choke coils, others are transformers—we will study both.

**Impedance Coupling.** Essentially, an impedance-coupled amplifier is like a resistance-coupled amplifier except for the substitution of one or more iron-core choke coils for the resistors. Fig. 11A shows a full impedance-coupled amplifier. Here choke coil  $L_1$  is used as the plate coil, and choke coil  $L_2$  is used as a grid coil for tube  $VT_2$ . The operation is similar to that of re-

sistance coupling except for the effects of the coils on the frequency response, and the effect of  $L_1$  on the plate voltage.

Since  $L_1$  has a low d.c. resistance, there will be very little d.c. voltage drop across it. Practically the full supply voltage is applied to the plate of the tube. For this reason, this circuit is particularly useful where the B supply is very limited, as in battery-powered circuits.

Coil  $L_2$  also has a low d.c. resistance. Therefore, any gas current flowing through  $L_2$  will cause but a small voltage drop, so the use of a coil eliminates the bias shift encountered when a grid resistor is used with a gassy tube.

► Since both choke coils offer higher reactances as the frequency increases, we might expect the gain of the stage to go up as the frequency rises. However, good high-frequency response is not obtained, because the choke coils have rather high distributed capacities, which are effectively in parallel with the coils. The distributed capacity tends to cut off the high-frequency response even more rapidly than in a resistance-coupled amplifier, because the coil capacities are added to the normal shunting capacities in the circuit.

The low-frequency response is poor also, because the reactance values drop at low frequencies. Hence, unless very large values of inductance are used, the low-frequency response will be much poorer than that of the mid frequencies.

Fig. 11B shows a variation of this circuit in which coil  $L_2$  is replaced by resistor  $R_2$ . This eliminates the distributed capacity and inductance troubles of one of the choke coils, so this circuit is somewhat better in frequency response than that shown in Fig. 11A.

This is the impedance-coupled circuit most likely to be found in use, for it is considerably cheaper than the one in Fig. 11A.

Fig. 11C shows another possible variation, in which coil  $L_1$  is replaced by resistor  $R_1$ . (Choke  $L_2$  is used as the grid coil.) This circuit has little to recommend it unless tube  $VT_2$  is likely to be gassy and a high resistance is not wanted in the grid circuit.

**Transformer Coupling.** Fig. 12 shows an example of a transformer-coupled voltage-amplifier stage. As you learned in an earlier lesson, transformers have a special kind of amplification also; they can step up the signal voltage by their turns ratio.

Therefore, if tube  $VT_1$  in Fig. 12 has a gain of 10, and the transformer  $T_2$  a step-up ratio of 3, the first stage gain will be the product of the two, or 30. Hence, transformer-coupled amplifiers give much higher gain for the same type of tube than do either impedance-coupled or resistance-coupled amplifiers.

As you learned in an earlier lesson, the frequency response of a transform-

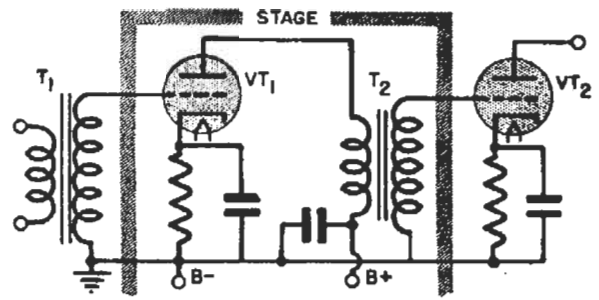


FIG. 12. A typical transformer-coupled, low-frequency, amplifier stage.

er is limited. The inductance of the primary winding must be very high to prevent an excessive loss of low frequencies because of the voltage division between the primary and the plate resistance of tube  $VT_1$ . In addition, the distributed capacity of the windings must be low to prevent an excessive loss of the high frequencies. Essentially, transformers give a frequency response similar to that obtained with impedance coupling.

► The resistance-coupled amplifier offers far better fidelity than either of the devices using iron-core coils. However, the high amplification obtainable from the transformer makes it a favorite where gain is more important than frequency response.

## Single-Ended Power Amplifiers

Once the voltage amplifier has made the signal sufficiently large, the voltage is fed into a power stage which supplies the power to drive the reproducer (a loudspeaker in a sound receiver). On paper, the power stage diagram is very similar to that of the other audio stages. It is not until we notice the plate current values and bias voltages that we see the difference.

Modern receiver loudspeakers require a considerable amount of a.f. power—anywhere from 1 watt to 12 watts on maximum output levels. Ord-

nary *voltage* amplifying tubes cannot furnish anywhere near this power. Most of them draw only from .25 watt to about 1 watt of d.c. power. This power is found by multiplying the B supply voltage by the d.c. plate current. For example, if the B supply voltage is 250 volts, and the d.c. plate current is 1 ma. (.001 amp.), then the d.c. power is  $250 \times .001$ , or .25 watt.

The total developed a.f. power is always far less than the d.c. power, and at least half the a.f. power is lost in the plate resistance of the tube. There-

fore, we must use an output tube capable of delivering a higher power than can a voltage amplifier.

This means a power tube must draw a higher d.c. power than a voltage amplifier in order to deliver the required a.c. power. Since it is desirable to operate all the stages at the same plate voltage to simplify power pack

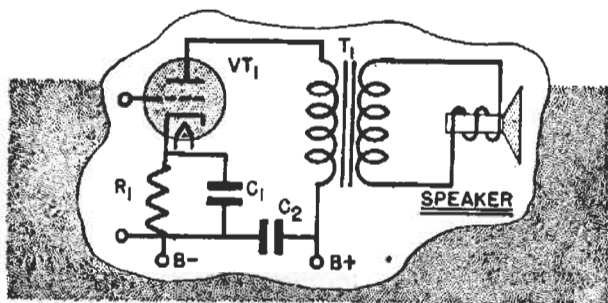


FIG. 13. The voice coil of the loudspeaker is matched to the plate impedance of the output tube by the output transformer.

design, power tubes are designed to draw more plate current. (Power is equal to voltage times current, so increasing the current increases the power.)



► To get the increased emission, the size (length and diameter) of the cathode is increased, and the filament current is increased to the value needed to heat the larger cathode. Then, the plate area is increased to correspond to the increased cathode size. This provides more electron paths (in parallel) from the electron cloud to the plate, and, as the same plate voltage acts across each, this has the effect of resistance in parallel—there is less plate-cathode resistance, so the plate current is higher for the same plate voltage.

For comparison, audio voltage amplifying tubes in radio receivers draw currents of from .5 ma. to perhaps 5 ma., but power output tubes draw currents of 30 to 50 ma. and more.

**Coupling to Speaker.** Fig. 13 shows the method of coupling from the plate of a power tube to the voice coil of a dynamic loudspeaker. Usually a

voice coil has an impedance of only 4 to 8 ohms, which is far lower than the plate resistance of the tube. Transformer  $T_1$  is used to match the two impedances.

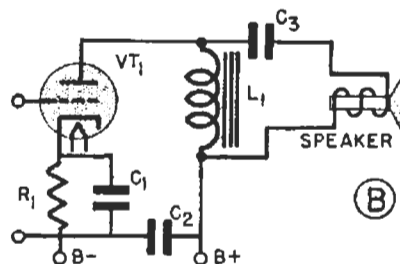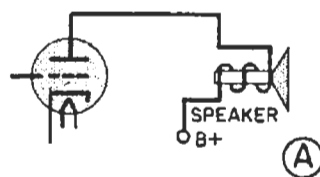**Load Matching.** As you know, maximum power output is obtained when the load impedance exactly matches the plate resistance of the tube. This does not assure minimum amplitude distortion. However, you will recall that increasing the load re-



Magnetic speakers were once very popular, and in radio servicing you may still encounter a receiver using one. An output transformer is not needed with them—they are made with many turns of wire, so it is possible for them to have impedances of 2000 to 6000 ohms, which is a close match to the required load for output tubes. In the direct coupling shown at A, the d.c. plate current flows through the speaker. This may be undesirable, for, if the wrong connections are made, the resulting d.c. flux will be opposite to that of the permanent magnet used in the speaker. This may ruin the speaker magnet. Also, the high current requires large wire sizes, which may make it difficult to wind the coil in the space provided. Hence, many sets used the choke-condenser coupling shown at B to avoid this; here the d.c. is blocked by  $C_3$  and flows only through  $L_1$ .

sistance value tends to flatten the triode tube characteristic curve. Therefore, it has been found that with triode tubes, a load equal to about twice the plate resistance value will give the maximum *undistorted* power output.

Notice the difference. The maximum power, with some distortion, is ob-



tained when the load and source values are matched. The maximum *undistorted* power (less than the maximum power but with less distortion) is obtained when the load is twice the tube resistance. (Further increasing the load resistance reduces the distortion some more, but the power output falls off because of the mismatched impedances.)

The load values and operating voltages listed in tube charts for triode power tubes are for the *maximum undistorted* power output, and the output transformer is designed for these values.

## PENTODE AND BEAM POWER-OUTPUT TUBES

The triode power-output tube offers very good fidelity, but it requires a high signal input to be driven to its full output. Also, it consumes a considerable amount of d.c. power. The latter is no problem in a large receiver with a heavy-duty pack, but is troublesome in a set using battery or a.c.-d.c. supplies, which are limited in their power. For these reasons, pentode and beam power tubes having higher efficiencies than triodes\* were developed.

The pentode and beam tube types require considerably less grid signal voltage than does a triode to produce the same output. For example, the type 2A3 triode tube requires a grid signal having a peak value of nearly 45 volts to give 3.5 watts output. On the other hand, the 6K6G pentode power tube requires a signal of only

\* For comparison, the a.c. power output (with permissible distortion levels in the case of the pentode) of the 6K6G pentode and the 2A3 triode are similar (about 3.5 watts). With the same plate voltage, the 2A3 draws 60 ma., but the 6K6G draws only 32 ma. The d.c. powers used, at 250 volts, are 15 watts for the 2A3, and 8 watts for the pentode.

about 18 volts peak to give 3.5 watts output.

This is important because it leads to a simpler voltage-amplifier design. In most receivers, one voltage-amplifier stage is plenty with pentode or beam output tubes, but triode output tubes frequently require two.

**The Pentode Tube.** Fig. 14 shows an output stage using a typical power pentode tube. As you will notice, this tube has three grids. From the cathode toward the plate, these grids are, respectively, the control grid, the screen grid, and the suppressor grid.

The control grid performs the same

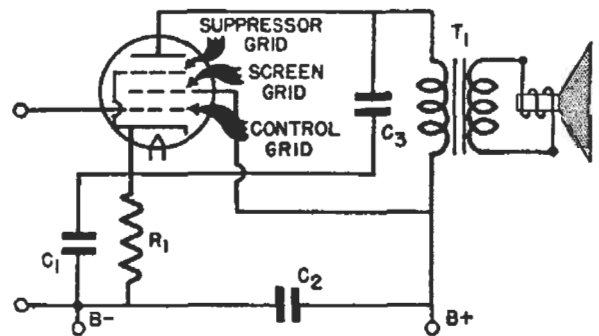


FIG. 14. The elements of a pentode power output tube are identified.

function as it does in a triode tube. ► The screen grid is a relatively coarse grid that is connected to a positive voltage—the screens of power types are usually connected directly to B+. Its high potential causes it to draw electrons from the electron cloud. The screen grid catches some of these, but because of its coarse structure (widely separated turns of wire) most of the electrons go through the mesh to the plate.

Since the screen grid is considerably closer to the cathode than the plate is, the plate current is much more dependent on the screen grid voltage than it is on the plate voltage. If the screen grid voltage is kept constant, the plate voltage can be varied over rather wide

limits without changing the plate current to any considerable extent.

Hence, in pentodes, the control grid has far more effect on the plate current than does the plate voltage, so the pentode has a high amplification factor. (As you know, the amplification factor or  $\mu$  of a tube is the ratio of the plate voltage change to the grid voltage change that produces the same plate current change.) This means that to obtain the same a.c. plate voltage ( $\mu e_G$ ) and hence the same a.c. power, the grid signal voltage required by a pentode is much smaller than that required by a triode power output tube. Thus, the *power sensitivity* of a pentode is much higher than that of a triode.

► The screen grid gives us the desired high sensitivity, but the presence of this second positive element causes a trouble that requires the presence of the suppressor grid.

The screen grid attracts electrons and speeds them on their way to the plate (in fact, it is sometimes called an accelerating grid). When these high-speed electrons strike the plate, other electrons are knocked out of the plate material. This emission of electrons due to bombardment is known as *secondary emission*.

As long as the plate is more positive than the screen grid, these secondary emission electrons are attracted right back, so no harm results. However, the voltage developed across the plate load varies with the signal, and, of course, this drop will at times be so large that the plate voltage (supply minus load voltage) falls below the screen grid value. Whenever this occurs, the secondary emission electrons tend to move from the plate to the more positive screen grid. This reversal of electron flow will reduce the plate current, causing distortion.

Secondary emission is not prevented by the suppressor grid, but its bad effects are removed. This grid, tied to the cathode, is always at the cathode potential. It is therefore always negative with respect to the plate, and repels any electrons that try to move away from the plate, driving them back. Only the slower-moving secondary emission electrons are controlled by the suppressor grid; the high-speed electrons moving from the electron cloud fly past this grid so fast that its potential cannot block them.

**Beam Power Tubes.** The beam power tube is practically a pentode tube. However, instead of a suppressor grid, it uses a pair of beam-forming electrodes to get the same effect. Fig. 15 shows a cut-away view of such a tube.

The beam-forming electrodes are connected to the cathode, so they are negative with respect to the plate. They repel electrons, forcing the electrons to "bunch together" and pass through the openings between these electrodes to reach the plate. Thus, they force the electrons to form two streams or "beams." This concentrates the flow of electrons in a stream, actually producing a compact mass of them between the plate and the screen grid. There-

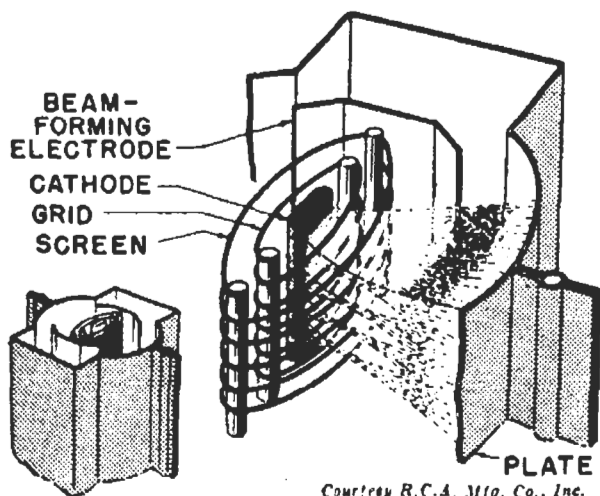


FIG. 15. The internal construction of the beam power output tube.

fore, any secondary emission electrons trying to move from the plate toward the screen grid are met at once by a large body of negative electrons (practically an electron cloud between the plate and the screen grid) that forces them back to the plate.

resistance of the 6K6G is about 50,000 ohms). Notice, too, that increasing the load resistance does not improve the shape of the characteristic. In fact, the opposite occurs; an increased load resistance increases the curvature at the right end of the dynamic curve.

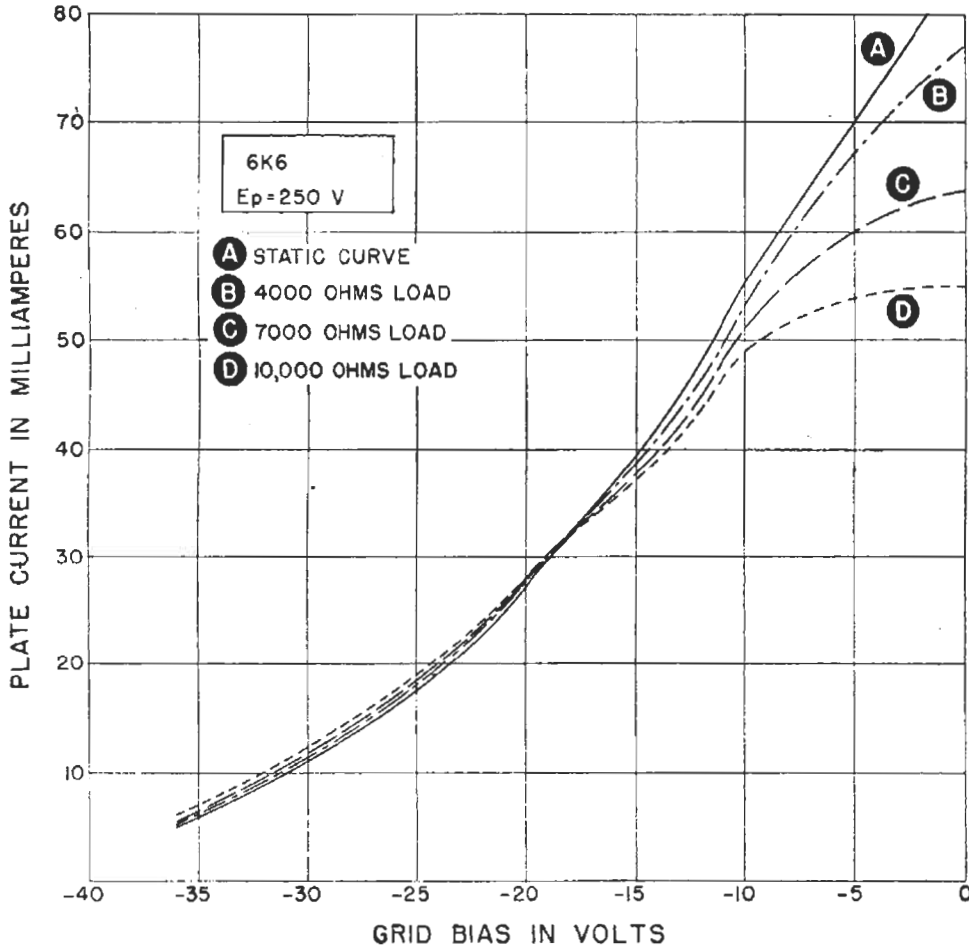


FIG. 16. These curves are typical of the static and dynamic curves of pentode power output tubes. Notice the upper bend curvature increases with load increases. Hence, the load must be kept low to keep down the third-harmonic distortion.

## PENTODE AND BEAM POWER DYNAMIC CHARACTERISTICS

The dynamic characteristics of pentode and beam power tubes are not as linear as are those of a triode. Fig. 16 shows the static curve for a typical pentode output power tube and also the dynamic curves for several load values.

Notice that the load values given in Fig. 16 are far below the plate resistance for the tube (the a.c. plate

This undesirable drop-off in the curve occurs because the plate voltage falls below a critical value. That is, the plate current of a pentode or beam power tube is relatively independent of the plate voltage until the load voltage drop causes the plate-cathode voltage to fall about 75 volts. Further reduction of the plate voltage causes the plate current to drop, too. Therefore, the plate current follows the grid voltage changes only up to this point where the plate voltage "takes over."

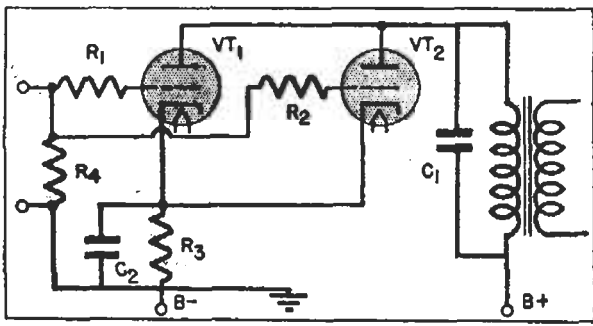


FIG. 17. Parallel output tubes were once commonly used to get an increased power output. However, the parallel arrangement is not ideal; it is subject to oscillation whenever the two tubes are not EXACTLY alike in their characteristics. (Aging will change them even if they were alike when new.) The feedback occurs through the grid-plate capacity of the tubes; to absorb this power, resistors  $R_1$  and  $R_2$  are sometimes added in series with the grids of the tubes as shown. These resistors do not have any current flow through them unless there is feedback current through the tubes. Any such feedback current must flow through the resistors, causing a loss of feedback energy. Sometimes resistors are necessary in the plate circuits as well, to prevent oscillation in the higher powered circuits.

The curves shown in Fig. 16 indicate that increasing the load does not remove all the second harmonic distortion, and actually increases the third harmonic distortion. (As you learned in an earlier lesson, second harmonics are added by operation over a single curvature, and third harmonics result if there is a double curvature in the tube characteristic.) Since third harmonic distortion is very distressing to the human ear, it is impossible to use a load value anywhere near the plate resistance value for this tube. Actually, the recommended load value is usually about one-seventh to one-ninth the plate resistance value for pentodes and beam power tubes.

The 6K6G tube, used with the recommended load value of 7600 ohms, will give us considerable power output, but the output will have a fairly high harmonic content when compared to that of a triode. Thus, a pentode will give us a greater power sensitivity and greater efficiency than a triode,

but only at a cost of increased distortion.

Beam power tubes are not quite as bad in this respect as are pentodes, but the triode can still give far better fidelity than either. However, the great power sensitivity of the pentode and beam tubes has made them widely used, and some of the limitations on their fidelity have been removed by a special circuit known as inverse feedback. We'll study this later in the Lesson.

## PREVENTING OSCILLATION

You may have wondered at the use of  $C_3$  in Fig. 14. In most circuits we try to *avoid* plate-to-cathode capacity, since it reduces the high-frequency response. However, particularly in power stages using pentode and beam power tubes,  $C_3$  is necessary to prevent oscillation.

The power output stage has rather high load voltages, so even a small percentage of feedback to the grid circuit may supply enough power to allow the stage to oscillate. Furthermore, the leakage inductance of the output transformer makes the plate load inductive. This means the load voltage is in the proper phase to cause oscillation if it is fed back to the grid circuit.

The frequency of the oscillation may be well above the audible range because resonant circuits are formed by the long leads and the stray capacities in the stage. However, regardless of the frequency of oscillation, the circuit will be blocked and signals cannot pass.  $C_3$  is an effective by-pass at these high frequencies and reduces the feedback enough to prevent oscillations.

Since the larger the capacity of  $C_3$  is, the more it will by-pass the higher audio frequencies, the smallest value that will adequately prevent oscillation

tion is used. Commonly used values range from .001 mfd. to .02 mfd.

Usually, the set is designed so that  $C_3$  and the output transformer resonate near the high-frequency end of the pass band and thus prevent some of the drop-off at these frequencies.

In some receivers,  $C_3$  may be connected directly across the primary of  $T_1$ , or else its lower end may go to the chassis instead of to the cathode. These changes do not affect the results as long as  $C_2$  and  $C_1$  are effective.

## PARALLEL OUTPUT TUBES

When more power output is needed than can be obtained from a single tube (and a more powerful tube is not available or is undesirable because of voltage requirements), more than one output tube must be used. One way in which two or more tubes can be used is to connect them in parallel, as shown in Fig. 17. The corresponding parts—plates, grids, and cathodes—of the two tubes are tied together.

Since the plate resistance of the two tubes in parallel is only half that of

one tube alone, the load used is likewise only half the value that would be used with a single tube. Both tubes furnish current, so the load current is doubled. The result is that the power output of this parallel arrangement is twice that of a single tube for the same applied signal voltage.\*

However, the parallel output stage is unstable (oscillations occur easily), and the fidelity is no better than that of a single output tube. When another arrangement, known as the push-pull connection, was developed, the parallel circuit was abandoned for receivers. The push-pull circuit provides even more power from two tubes than does a parallel connection and gives better fidelity. We'll study this circuit next. ► Incidentally, to distinguish between the push-pull and other connections, any power stage using a *single* tube or *parallel* tubes is known as a *single-ended* stage. The *push-pull* stage is called a *double-ended* stage.

---

\* The power is  $I^2R$ , so doubling the current would give four times the power, but halving the load resistance gives us a net of twice the output.

---

# Push-Pull Power Stages

The maximum power output that can be usefully obtained from a tube depends on the amount of distortion permissible. The push-pull circuit is particularly desirable because it eliminates all even harmonics that result from amplitude distortion in this stage. Thus, it has far better fidelity than does the single-ended output stage. This leaves only the odd harmonics so the power output can be increased until the odd-harmonic distortion level becomes objectionable. In fact, it is possible with the push-pull circuit to

obtain considerably more than twice the undistorted power that a single tube could deliver.

Essentially, a push-pull circuit is one in which the grids of two tubes are fed out of phase, and the resulting plate currents are recombined so that any *even* (second, fourth, etc.) harmonics *that are produced by distortion in the stage* are cancelled. (It is important to realize that any harmonics *that are part of the signal* will pass through the stage; it is only harmonics *added within the stage* that are can-

celled.) This circuit is used with triode, pentode, and beam power tubes; we'll take up each in order.

### TRIODE PUSH-PULL STAGES

The basic triode push-pull circuit is shown in Fig. 18. Tubes  $VT_1$  and  $VT_2$  are identical types. The plate supply is fed through the center tap of transformer  $T_2$ , so that the plate current of  $VT_1$  flows through one half of the transformer while the plate current of  $VT_2$  flows through the other half. Bias is obtained as a result of the flow of the combined plate currents through  $R_1$  from B— to the cathodes.

The grid circuits are completed through the secondary of transformer  $T_1$  to its center tap, where the return circuit goes through ground to  $R_1$ .

► Notice the direction of the electron flow in each plate circuit, as indicated by  $i_1$  and  $i_2$ . In each tube, electrons move from cathode to plate. Therefore, the two d.c. plate currents flow in *opposite directions* through halves of transformer  $T_2$ . Assuming we have identical tubes with the same bias and no signal, these plate currents are practically equal. Therefore, since the plate currents are equal in value, and flow in opposite directions through  $T_2$ , the fluxes produced by these *d.c. currents* cancel each other, and no resulting flux exists in the transformer core when there is no signal. (When current flows one way through a transformer, the flux lines in the core have a particular direction. When the current is reversed, the flux direction reverses. Therefore, if *equal* currents flow through equal windings in opposite directions, the two fluxes cancel each other.)

**Tracing The Signal.** Now let's assume that a sine-wave signal  $e$  is applied to the primary of transformer  $T_1$  in Fig. 18. A larger voltage will ex-

ist across the secondary, since this is a step-up transformer.

The induced voltage exists across the entire secondary winding of  $T_1$ . Therefore, when terminal 1 of the secondary of  $T_1$  is positive, terminal 3 must be negative, and vice versa.

► For the moment, let's assume that terminal 1 is positive. Then, the voltage  $e_1$  between terminals 1 and 2 is that applied to  $VT_1$ . This is half the total voltage, and at the moment, the grid end of the winding is positive. Therefore, at this instant, the positive signal voltage makes the grid of  $VT_1$  less negative (it subtracts from the bias voltage), so the plate current of  $VT_1$  increases.

At the same instant, terminal 3 is negative with respect to terminal 1. In fact, it is the most negative point on the winding, so the voltage  $e_2$  (between 2 and 3) is negative. This signal voltage adds to the bias, making the grid of  $VT_2$  more negative, so this tube's plate current decreases. Thus, you can see that the two grids are fed signals that are  $180^\circ$  out of phase, because when one is positive the other is negative.

Since on this half-cycle the current

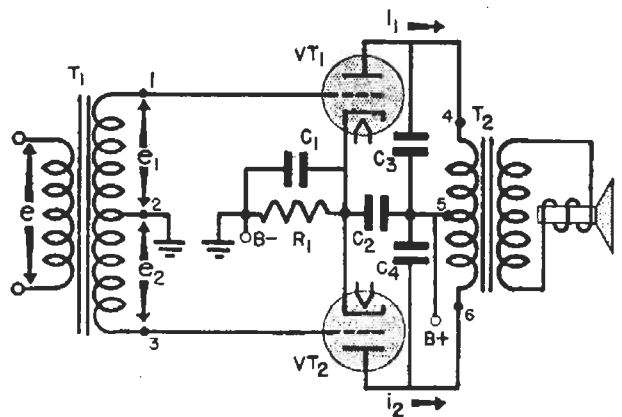


FIG. 18. A typical triode push-pull stage. In some cases you may find that by-pass condensers  $C_1$ ,  $C_3$ , and  $C_4$  may not be used in push-pull stages of this type. Condenser  $C_1$  is not required if the tubes are balanced (as you will see when you study inverse feedback), and  $C_3$  and  $C_4$  are needed more with beam power tubes than with triodes.

$i_1$  of tube  $VT_1$  is increased, and at the same time the current  $i_2$  of  $VT_2$  is decreased, we get an important action in the transformer  $T_2$ . This changing plate current has an a.c. component, so an a.c. voltage is produced across the primary of  $T_2$ . Let us say that terminal 4 is becoming more positive than 5, while 6 is becoming more negative than 5. Hence, terminals 4 and 6

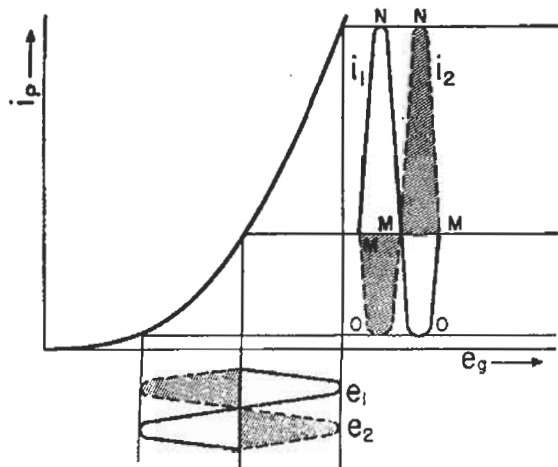


FIG. 19. When the operating point is on the lower bend of the tube's characteristic, the plate current pulses  $i_1$  and  $i_2$  will be distorted.

are opposite in polarity. *Insofar as the entire primary is concerned, therefore, the two voltages add together and act like a single a.c. voltage of twice the value of either component.* Also, the resulting a.c. current in the primary causes an a.c. flux in the core, which in turn induces a voltage in the secondary of  $T_2$ .

► In the next half-cycle the polarities of  $e_1$  and  $e_2$  are interchanged (but they stay  $180^\circ$  out of phase) so the two actions reverse: current  $i_1$  now decreases and  $i_2$  increases. This reverses the phase of the a.c. voltage across the primary of  $T_2$  and so reverses the direction of the flux in the core.

Since the a.c. voltage across the primary of  $T_2$  is produced by *two* tubes, it is twice the value produced by one tube; in other words, we have double the power output of a single tube.

However, it is possible to get more from this stage, because distortion is reduced to the point that a greater output is obtainable. Let's see how.

**Distortion Cancellation.** Let's again apply a sine-wave signal and operate near the lower bend of each tube's characteristic curve, as shown in Fig. 19. Considering first the grid signal  $e_1$  shown by the solid-line curve, the corresponding plate current curve is  $i_1$ —also shown by a solid curve. The plate-current wave shape is not equal in amplitude on the two sides of its zero axis—that is, the alternation  $M-N$  is greater than the alternation  $M-O$ —so we have added the second and other even harmonics to the original fundamental sine wave.

At the same moment the other tube is getting the grid voltage  $e_2$ . Therefore, as shown by the dotted lines in Fig. 19, its plate current  $i_2$  is distorted also on the  $M-O$  alternation. However, since  $e_1$  and  $e_2$  are  $180^\circ$  out of phase, the plate current alternation of  $i_1$  that is distorted occurs at the same moment as the portion of  $i_2$  that is *not* distorted (and vice versa).

► Now let's examine the action occurring in  $T_2$  when these plate currents flow in the primary. As shown in Figs. 19 and 20, the plate currents  $i_1$  and  $i_2$  are  $180^\circ$  out of phase. However, remember that they flow in *opposite directions* through the halves of the primary of  $T_2$ . Therefore, if  $i_1$  produces flux  $f_1$  as shown in Fig. 20, then  $i_2$  will produce the flux  $f_2$ . In effect, the reversal of plate current direction through the primary has resulted in  $f_2$  being "flipped over." And, as we explained earlier, the two fluxes add together as if they were produced by a single a.c. voltage across the entire primary winding. Hence, when  $f_1$  and  $f_2$  in Fig. 20 are added (thus,  $A-B$  plus  $C-D$  equals  $E-F$ ), the resultant flux

$f_c$  is NOT AS DISTORTED as are  $f_1$  and  $f_2$ . The second-harmonic distortion present in the plate currents has been eliminated by the action of the fluxes in  $T_2$ .

► Also, the same cancellation will occur on any other even harmonic, so no even-harmonic distortion of any consequence is produced in a push-pull stage. (IMPORTANT: Harmonics in

$f_2$  has exactly the same shape. Adding the two together reinforces the odd harmonics instead of producing cancellation. The resultant  $f_c$  thus is just an enlarged version of its two components and contains just as many third harmonics (or other odd harmonics).

**Summary.** We can then say about push-pull circuits:

1. The d.c. plate currents are equal and opposite, so the d.c. fluxes in  $T_2$  cancel.

2. The a.c. plate currents are  $180^\circ$  out of phase, but since the currents flow in opposite directions through  $T_2$ , the fluxes add in the core of the transformer.

3. If even harmonics are added by amplitude distortion in the push-pull stage, they are wiped out when the fluxes are added in the output transformer.

4. If odd-harmonic distortion occurs in a push-pull stage, no cancellation exists—odd harmonics go through the


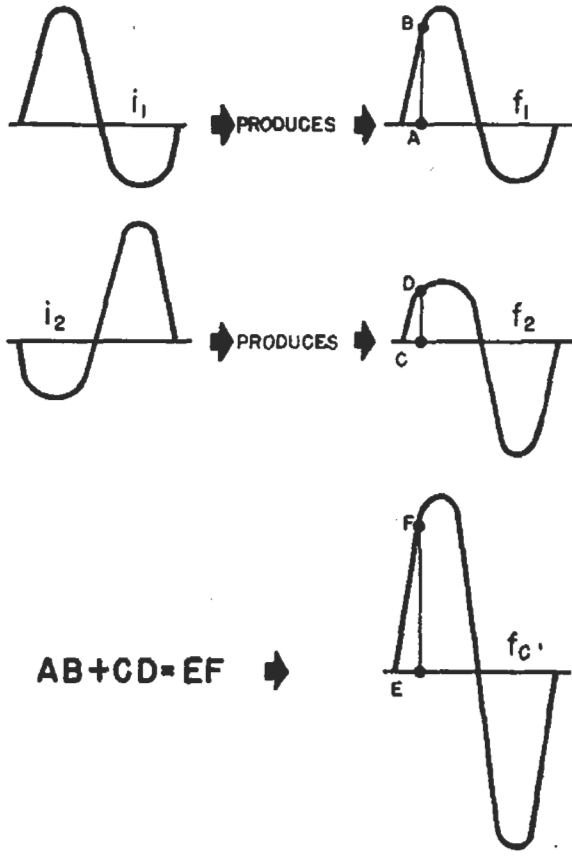


FIG. 20. The even-harmonic distortion cancellation occurs because of the manner in which the fluxes add in the output transformer.

the original signal are not cancelled, because they act like any original signal applied to the push-pull stage. This action occurs only for harmonics added by the push-pull tubes.)

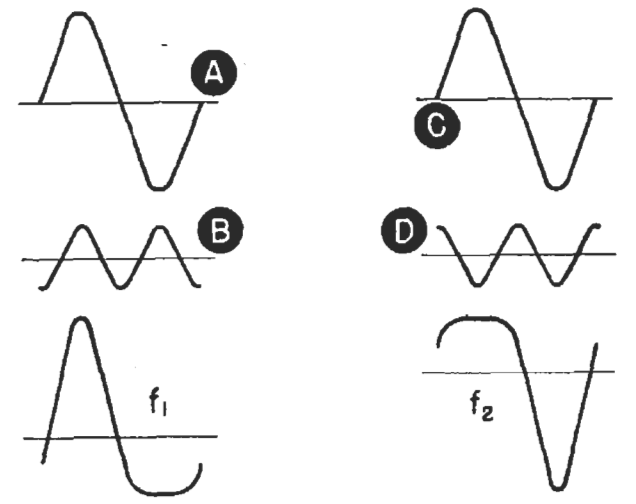**Third Harmonics.** Third harmonics are not cancelled, because odd-harmonic distortion affects both halves of the flux cycle, and adding the two flux components would not remove the distortion. This is shown in Fig. 21. Flux  $f_1$  has a square-top shape (indicating odd harmonics have been added), and



Perhaps the second-harmonic cancellation can be seen easier by considering the components of the fluxes. Flux  $f_1$  is the result of adding a fundamental A to a second harmonic B that is  $90^\circ$  out of phase with it. Similarly,  $f_2$  is the result of combining the fundamental C with the  $90^\circ$  out-of-phase second harmonic D. With  $f_1$  and  $f_2$  in the relationships shown, you can see that the fundamentals A and C are in phase and can be added directly. However, the second harmonics B and D are  $180^\circ$  out of phase with each other, so they cancel each other.



circuit in the same way as the fundamental wave.

► These facts are true whether the even and odd harmonics are the second and third or are the sixth and seventh—all *even* harmonics are eliminated, and *odd* harmonics are passed on.

Triode tubes have considerably more *even*-harmonic distortion than

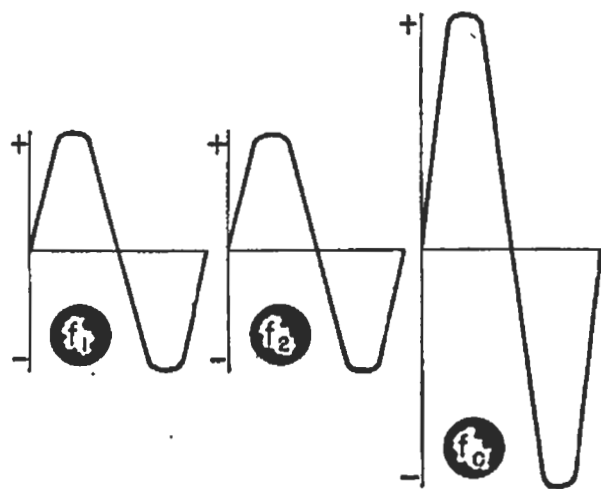


FIG. 21. Odd-harmonic distortion is not cancelled in push-pull circuits because both halves of the flux cycle are distorted, so when they are added, the combination must have the same distortion.

*odd*-harmonic distortion. Therefore, the push-pull circuit arrangement with triode tubes in a class A amplifier comes very close to the ideal in giving distortionless output.

**Increasing the Output.** The elimination of even-harmonic distortion in a push-pull stage permits us to get an undistorted output from the stage, that is more than twice as large as the undistorted output a single tube can give. We can get this greater output by doing two things:

1. We can make the load more nearly equal to the plate resistance.

2. We can adjust the bias so that the operating point is nearer the lower curved section of the characteristic, thus permitting a larger grid signal voltage, which in turn means a greater plate-current swing and more a.c. power.

Of course we could take both these steps with a single-tube amplifier, but doing so would increase the even-harmonic distortion in the amplifier. Such increased distortion also occurs in the push-pull stage, but the action of the stage promptly wipes it out; as a result, we get increased power without increased even-harmonic distortion. We can get about 2.5 times as much output power from a push-pull stage as from a single-ended stage before odd-harmonic distortion begins to become objectionable.

## PENTODE AND BEAM POWER PUSH-PULL STAGES

Pentode and beam power tubes are used in push-pull arrangements in the same way that the triode is. As shown in Fig. 22, the only difference is the substitution of a pentode (or a beam

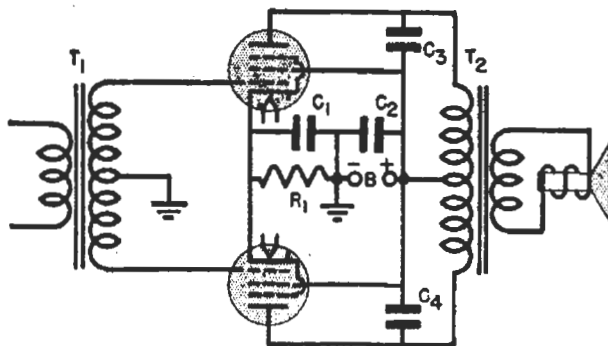


FIG. 22. A pentode push-pull power output stage.

power) tube in place of each triode. The operation of the stage is essentially the same.

However, pentode and beam power tubes have greater amounts of distortion, particularly third-harmonic distortion. Therefore, with push-pull stages using these tubes, it is common practice to use a low-resistance load.

As was shown for the 6K6G tube in Fig. 16, a small load causes less odd-harmonic distortion because it causes less of a bend in the dynamic curve

at the right-hand end. Such a load may cause more bend in the lower part of the characteristic, and thus cause more even-harmonic distortion—but we don't care; the even-harmonic distortion is eliminated by the push-pull arrangement.

In practice, a load resistance value is chosen to give all the power possible at the permissible value of odd-harmonic distortion. If, say, 5% third harmonic is permissible, the load resistance value is increased (thus increasing the power output) until the third-harmonic distortion reaches this value.

### CLASS B PUSH-PULL STAGES

The circuits we have just discussed have been adjusted for class A operation. The operating point is chosen so that the grid will never be swung positive, nor will the plate current ever be zero.

However, where high power and high efficiency are required, a *push-pull* circuit can be operated as a class B amplifier (that is, operated with a bias set at the plate current cut-off point) without creating excessive distortion. As Fig. 23 shows, operating the tubes with the bias at the cut-off point causes the plate currents to be half-wave pulses. Then (Fig. 24) the flux produced by the other will fill in the spaces. The combination produces the complete a.c. flux cycle  $f_c$ . In other words, one tube works on one half-cycle, and the other tube works on the other half-cycle in the class B push-pull stage.

The class B stage has an increased efficiency because each tube operates for only half of each cycle and passes practically no current the other half-cycle. Thus, there is no steady d.c. plate current to cause a constant power loss in the plate resistance of the tube.

This is important because the amount of power that can be delivered from a stage depends on the ability of the tube to dissipate the heat developed within it. Thus, if a tube can dissipate 5 watts safely, we can increase the output only to the point where this power is lost in the plate resistance. Therefore, if we reduce the loss, we can safely increase the grid signal voltage, to where the same loss occurs.

This is exactly what happens in a class B stage. Reducing the average plate power by causing the plate current to exist for only half the time permits the grid signal level to be increased (the grid can even go slightly positive). In turn, this produces high plate current pulses, so a large amount of a.c. power is delivered to the load. Since operation requires a specially designed voltage amplifier, the entire system must be designed for it. Fur-

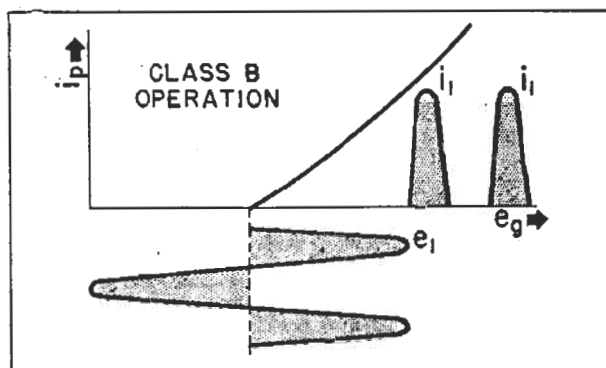


FIG. 23. Class B operation is at the plate current cut-off point, so the plate current pulses exist for half cycles.

thermore, class B operation in the low-frequency amplifier is possible ONLY in a push-pull circuit—otherwise half the signal would be destroyed.

► On paper, a class B stage looks much like a class A push-pull circuit. However, a fixed bias from the power supply is always used instead of self-bias, unless special zero-bias class B tubes are used. (Some class A stages use fixed bias also.) With a fixed bias

instead of  $R_1$ , Fig. 22 could be a class B stage, providing the following parts differences are considered:

Transformer  $T_1$  will be a step-down transformer, so its secondary will have low reactance. This is necessary because the grid is driven positive part of the time in class B operation, causing a grid current flow. If the trans-

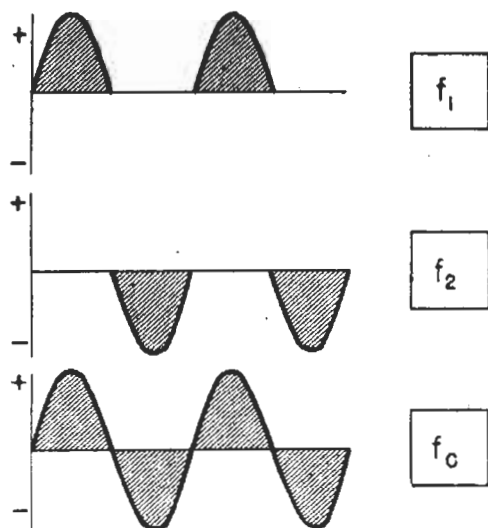


FIG. 24. As shown here, class B push-pull operation causes the tubes to supply current pulses alternately. The corresponding fluxes add to reproduce the entire a.c. cycle.

former had high reactance, the grid current flow through it would cause a voltage drop in the transformer, that would distort the peaks of the applied signal. Since the grids draw current, the grid circuit requires power—it is not just voltage-driven. Therefore, the

preceding stage must be capable of furnishing this power, and the transformer  $T_1$  must be an impedance-matching type. A low-power tube (in a class A circuit) is frequently used ahead of a class B amplifier. This tube is known as the “driver” tube, because it *drives* the class B stage to its normal operating point.

The class B amplifier delivers more power than is usually necessary in a home receiver. For this reason, true class B amplification is rarely found except in public address systems or in other applications requiring high power. However, class AB operation, in between class A and class B amplification, is found in many of the more powerful home receivers.

### AB OPERATION

Class AB operation uses a C bias somewhere in between the cut-off bias of class B operation and normal class A bias. Then, if the driving voltage is limited so that the grid never becomes positive, the operation is known as class  $AB_1$ . On the other hand, if the signal voltage applied to the grid is permitted to go slightly positive (approaching class B operation) the operation is known as class  $AB_2$ . Class  $AB_2$  operation delivers higher power than  $AB_1$  but less power than does class B.

## Inverse Feedback

The output of any amplifier using pentode or beam power tubes contains a considerable percentage of distortion. One effective method of reducing this distortion (and also reducing any excessive hum, oscillation, or noise) uses the principle of inverse feedback.

Feedback, as the name implies,

means feeding part of the output voltage of an amplifier back into its input circuit. If the feedback voltage arrives at the input exactly in phase with the original input voltage, we have positive feedback, often called *regeneration*. If positive feedback is carried far enough in an amplifier, the amplifier becomes

unstable and finally oscillates.

For *inverse feedback* or *degeneration*, the phase relation between input and feedback voltages is such that the feedback voltage is made to arrive  $180^\circ$  out of phase with the input signal. This means that whenever the input signal rises in a *positive* direction, the feedback voltage rises in a *negative* direction, and vice versa. The feedback voltage, therefore, always opposes the original input signal. The resultant input is the difference between the two voltages, so it is always smaller than the original signal.

Since inverse feedback *reduces* the effect of the original input voltage, it reduces the output also. This amounts to a reduction in the amplifier gain. (An important point to remember is that unlike positive feedback, which makes an amplifier unstable and sometimes causes oscillation, inverse feedback drops the gain and output, making the amplifier entirely stable and always under control.)

So far, the only result of inverse feedback we have seen is a reduction in gain. Let us see what benefits this sacrifice may offer.

## REDUCTION OF DISTORTION

Let us examine the circuit in Fig. 25. Except for the inverse feedback connections, it is a conventional single-ended power amplifier. Note that the lower end of input transformer  $T_1$  is not returned to ground, but is connected to voltage divider  $R_1$ - $R_2$  across the secondary of output transformer  $T_2$ . (Resistors  $R_1$  and  $R_2$  are large in value compared to the impedance of the loudspeaker voice coil, so they absorb very little power from the circuit.) With this arrangement, part of the output voltage is fed back into the grid circuit; the exact amount of voltage can be regulated by adjusting the

values of resistors  $R_1$  and  $R_2$ .

Now, what happens when an input signal is applied to the circuit? First, the input signal  $e_1$  produces in the secondary of  $T_1$  the grid voltage  $e_2$ , which after amplification appears in the output as  $e_0$ . For simplicity, let us assume that although  $e_2$  is a pure sine-wave input voltage as in Fig. 26A, the output  $e_0$  looks something like that in Fig. 26B. The "bump" on the output wave may represent noise, distortion, or hum (or all three) generated in the amplifier tube. The bump thus represents something that should be eliminated, because it was not present in the original signal.

Through our feedback circuit, a portion ( $e_3$ ) of the distorted output  $e_0$  is fed back to the grid in series with  $e_2$ . This  $e_3$  voltage is indicated by the dotted curves in Figs. 26B and 26C.

For our purpose, we can assume that all these things occur instantaneously;

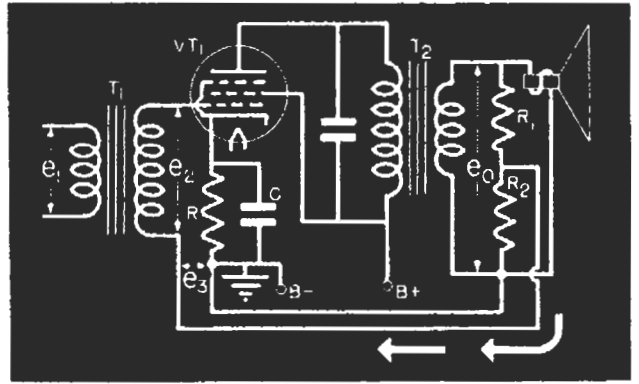


FIG. 25. A typical single-ended power output stage utilizing inverse feedback. The portion of the output voltage across  $R_2$  is fed back as  $e_3$  into the grid circuit.

that is, there is no delay between the time  $e_2$  is applied to the grid, and the instant that  $e_3$  is fed back into the grid circuit.

Suppose we have connected the windings of output transformer  $T_2$  so that feedback voltage  $e_3$  arrives exactly  $180^\circ$  out of phase with input voltage  $e_2$ , as shown in Fig. 26C. This

means we have inverse feedback. Since  $e_2$  and  $e_3$  are of opposite polarity, the resultant input is equal to their difference. This input is illustrated by the curve in Fig. 26D which is obtained by subtracting  $e_3$  from  $e_2$  in Fig. 26C.

The final output caused by the new reduced input will be something like that in Fig. 26E. It is apparent that

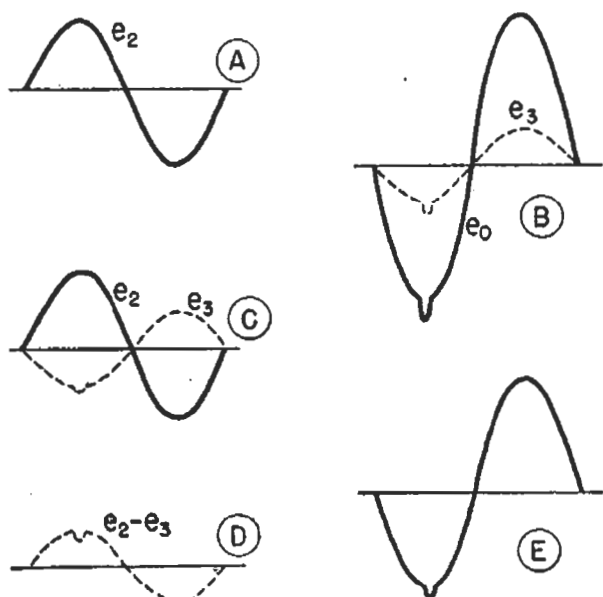


FIG. 26. These curves show how inverse feedback tends to correct amplitude distortion.

this is a much better reproduction of the original input than that obtained in Fig. 26B.

*Through the use of inverse feedback we have taken the amplitude distortion components of the output and put them back into the input in such a direction that they tend to cancel themselves.*

It is true that the output is reduced in amplitude in the process, because of the reduced effective input voltage (26D is smaller than 26A, so 26E is less than 26B,) but if the input signal voltage ( $e_1$  in Fig. 25) is increased, the output can be brought back to its former level while the distortion components remain substantially reduced.

The amount of reduction of all distortion, hum, and noise by inverse feedback depends upon the amount of output voltage fed back to the grid cir-

cuit and upon the gain of the amplifier without feedback. In general, the gain of an amplifier and the distortion in its output caused by the amplifier itself are reduced by an equal per cent. This means that if feedback voltage is increased until the gain has been reduced 50%, distortion will be reduced 50% also. If the input voltage is then doubled to return the output to its former value, the distortion in the stage will also double, but it will still be only 50% of what it would be without feedback.

► Suppose we have an amplifier that without feedback, has the frequency-gain characteristic curve 1 in Fig. 27. Let us say the poor response below 100 cycles is caused by coupling condensers that are too low in capacity, the peak at 3000 cycles by resonance effects in a transformer, and the loss of frequencies above 10,000 cycles by the shunting effect of tube capacities. Obviously, an amplifier with such a response would not give high-fidelity reproduction.

Now let us see what improvements inverse feedback might make. With a medium amount of output voltage fed back into the input in proper phase, we get response curve 2 in Fig. 27. This is a considerable improvement. Observe that although the over-all gain has been reduced, the low-frequency and high-frequency response is nearer the response of the intermediate range,

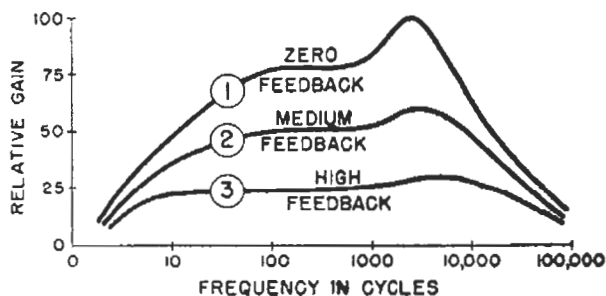


FIG. 27. Inverse feedback can also improve the frequency response, providing the gain can be sacrificed.

and the undesirable peak at 3000 cycles has been cut down.

How feedback brings this about may be visualized as follows: Below 100 cycles and above 10,000 cycles, where the amplifier's inherent gain is low, the output voltage also is low. This means the feedback voltage is small in magnitude, so the input is not reduced much. For the peak at 3000 cycles, however, the gain originally is high. The increased output voltage makes the feedback voltage quite large. When this is fed back, it cancels a large part of the original input and cuts the gain considerably. Therefore, the feedback corrects for frequency distortion as well as for amplitude distortion.

Even greater improvement in frequency response can be obtained if the value of the feedback voltage is increased, as in curve 3 of Fig. 27. Observe, however, that any increase in feedback is always accompanied by an additional reduction in gain. In-

single-ended stages. Let's study some of the typical circuits.

## TYPICAL INVERSE FEEDBACK CIRCUITS

In addition to the basic circuit you have just studied, there are a number of variations on the method of getting the required feedback. It is generally

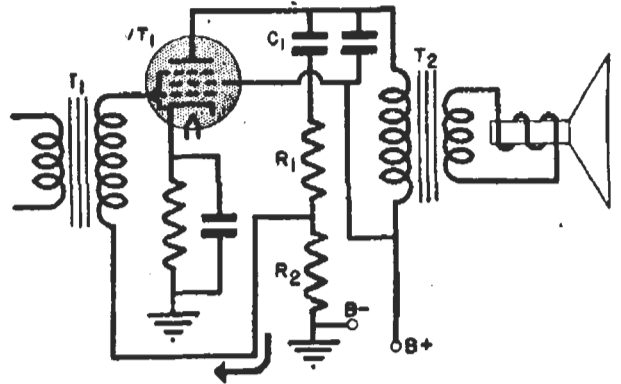


FIG. 29. Here the feedback is obtained from a voltage divider connected from plate to chassis.

unnecessary to feed back the entire output voltage to the grid circuit, and for this reason almost all feedback circuits use some form of voltage divider to reduce the feedback voltage. In the circuits shown in Figs. 28 to 32, the voltage divider resistors are marked  $R_1$  and  $R_2$ . The exact amount of feedback can be regulated by varying the resistance values.

► The output voltage developed across the average low-impedance loudspeaker voice coil (in a circuit like Fig. 25) does not always yield sufficient feedback voltage for satisfactory correction of distortion. However, an extra secondary winding having a greater number of turns can be added to the output transformer as in Fig. 28. This increases the feedback voltage with correspondingly better results.

► To get a high feedback voltage without an extra transformer winding, the voltage often is taken directly from

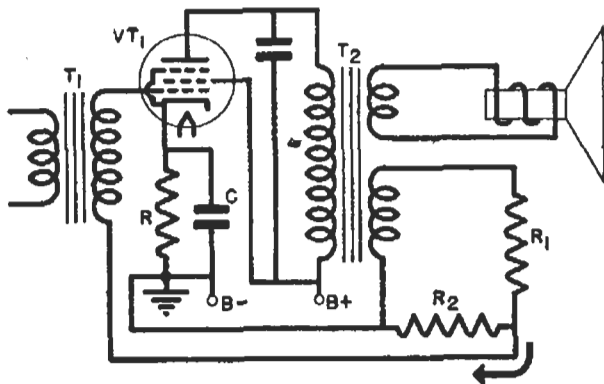


FIG. 28. Inverse feedback from a special winding on the output transformer.

verse feedback may be increased only to the point where it is impossible to get enough driving voltage (or where it becomes uneconomical to go further).

► The remarkable ability of inverse feedback to reduce distortion has resulted in its widespread use in modern receivers that use pentode and beam power tubes, particularly those using

the plate of the tube (Fig. 29). Condenser  $C_1$  serves only as a blocking condenser to prevent short-circuiting the d.c. plate supply and prevent application of the plate voltage to the grid. The capacity of  $C_1$  should be high enough so that the reactance of the condenser is small compared to the resistance of  $R_1$  and  $R_2$ , otherwise the feedback will not be the same for all frequencies.

► The feedback voltage may be fed in *parallel* with the input instead of in series. This is usually done with resistance-coupled input circuits like that shown in Fig. 30. Note that  $R_2$  is not only part of the feedback voltage divider circuit, but it is also the grid resistor for the tube.  $C_1$ , as before, is only a blocking condenser.

► For feedback over two stages, the circuit in Fig. 31 is often used. Observe that the feedback voltage is inserted in the cathode circuit. The feedback could not be applied to the grid of the first tube because we have a phase

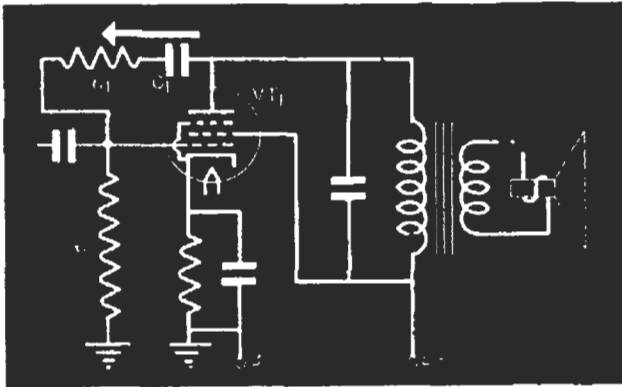


FIG. 30. The grid resistor  $R_2$  divides the feedback voltage with  $R_1$ .

shift of  $180^\circ$  in each tube, and with two tubes this makes a total shift between input and output of  $360^\circ$ . The voltage at the grid of the first tube, therefore, is exactly in phase with the output voltage, and coupling the feedback to the first grid would result in positive feedback.

► Feedback, however, can be applied to the grid of the first tube in a two-tube amplifier if an extra output transformer winding is used. Fig. 32 is an example of this. In this case, the connections to the extra transformer winding may be reversed, if necessary, for proper phasing.  $R_3$  serves only to load the transformer winding, and has no direct effect on the feedback voltage.

**Current Degeneration.** All the preceding systems are known as volt-

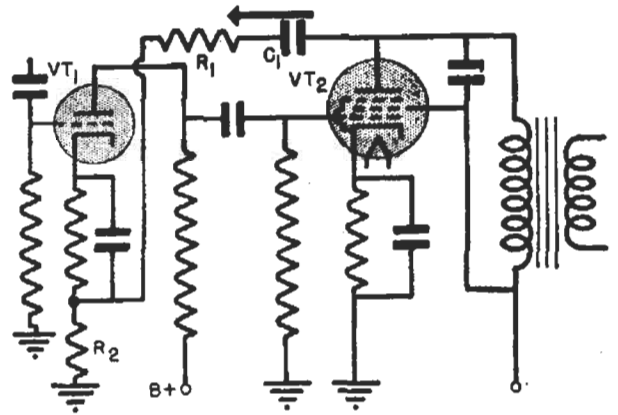


FIG. 31. Inverse feedback from the plate of the output tube to the cathode of a voltage amplifier.

age types, since it is the output *voltage* that is fed back. This system thus corrects the output voltage and hence reduces both frequency and amplitude distortion. There is another system which depends on the output tube plate *current*. This current type can correct for amplitude distortion but does not correct the frequency response.

A typical circuit is shown in Fig. 33. This is a conventional amplifier except that the bias resistor by-pass condenser has been omitted. With no condenser, the plate load consists of both the output transformer and the cathode resistor  $R_2$ , and a small part of the output voltage is developed as  $e_3$  across the cathode resistor. This voltage acts as a variable bias that opposes changes in the grid signal. When the grid voltage  $e_2$  goes positive, the increase in plate current through  $R_2$  increases the

bias ( $e_3$ ) and tends to make the grid more negative. When the signal swings negative, the bias  $e_3$  is reduced. Hence, it has the same effect as the inverse feedback circuits already described.

Since this circuit acts to minimize changes in plate current, it can correct amplitude changes but not the frequency response, because the same

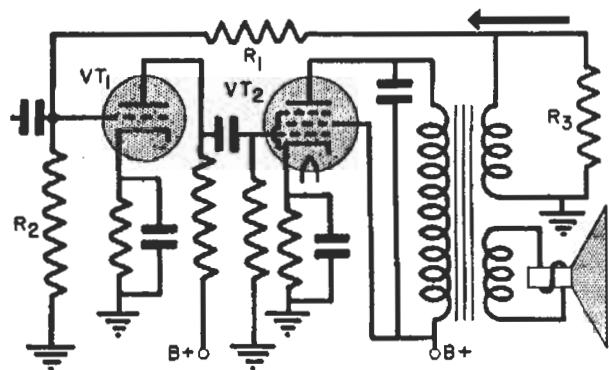


FIG. 32. Feedback from a special output transformer winding to the grid of a voltage amplifier.

plate current amplitude can cause differing output voltages if the load impedance changes with frequency.

### FEEDBACK LIMITATIONS

It has been assumed that the feedback voltage is always  $180^\circ$  out of phase with the input voltage in these feedback circuits. Unfortunately, this is not always true. In addition to the  $180^\circ$  phase shift in each tube, there is always some phase shift in each coupling condenser or audio transformer. These extra phase shifts are quite small at medium audio frequencies, but at extremely high and extremely low frequencies they can become quite large. When more than two stages are

included in the feedback path, it is possible that the net change in phase could result in positive instead of negative feedback, causing oscillation. Therefore, the design of these circuits must be carefully worked out. (It is necessary that any defective parts in these circuits be replaced by exact duplicates to avoid possible trouble of this kind.)

► All the inverse feedback systems shown here can be applied to push-pull stages as well. Incidentally, the cathode type of Fig. 33 introduces no degeneration in a push-pull stage (when the same resistor biases both tubes) unless the tubes become unbalanced. If the two tubes are the same, when one

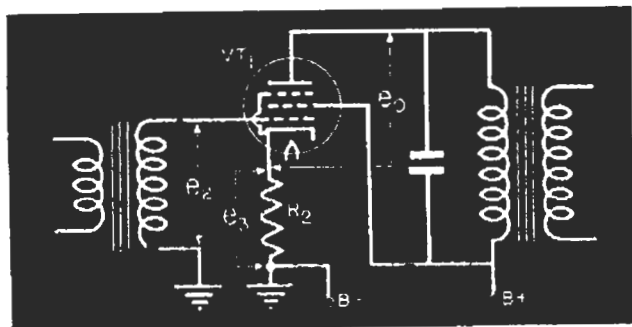


FIG. 33. Current degeneration is obtained when the cathode by-pass condenser is omitted. This will correct for amplitude distortion but not necessarily for frequency distortion.

plate current is increasing the other is decreasing, so the drop across the bias resistor is practically constant. Therefore, there will be no degeneration until the circuit is upset and needs it the most! For this reason, you will frequently find that the bias resistor for push-pull tubes is not by-passed.



# Phase Inverters

In our study of push-pull amplifiers, you undoubtedly noticed the use of two transformers. This was the standard circuit at one time. Modern practice, however, is to eliminate audio transformers whenever possible, since high-quality ones are bulky and expensive, and cheaper ones do not give faithful frequency response.

We can't, of course, get rid of the impedance-matching *output* transformer. (Nor, in class AB<sub>2</sub> and class B operation, can we avoid using the input transformer, for no other device can perform its two functions of offering low impedance and of matching impedances to the driver.)

However, in class A and class AB<sub>1</sub> operation, the *input* push-pull transformer is an ordinary voltage amplifying transformer whose only special function is providing a way to feed the two grids 180° out of phase. It can be eliminated if we can find some other way of doing this.

As you know, a vacuum tube stage reverses the phase of a signal 180° because the signal voltage across the load is opposite in polarity to the signal applied to the grid of a tube. Therefore, if we feed the grid of one of the push-pull tubes from a voltage amplifier, and then put in another tube (called a *phase inverter*) to reverse the phase to feed the other push-pull tube, we can have push-pull operation (class A) without using an input transformer.

A resistance-coupled stage is used as the phase inverter. Its use offers several advantages: higher fidelity characteristics, a reduction of the possibility of magnetic coupling and hum pickup, and a reduction in weight of the equipment. In general, it is cheaper to use a tube stage than the relatively expensive input push-pull transformer.

Of course, in addition to reversing the phase, the additional stage must not feed a greater signal to its push-pull tube than is fed to the other. Therefore, it is necessary to limit the gain so that the inverter tube will not have greater output than the voltage amplifier.

► Fig. 34 shows a simplified diagram of an inverter.  $VT_1$  is a voltage amplifying stage. It amplifies the signal, and feeds tube  $VT_2$  through the resistance coupling  $R_3$ - $C_4$ - $R_4$ - $R_5$ . A voltage di-

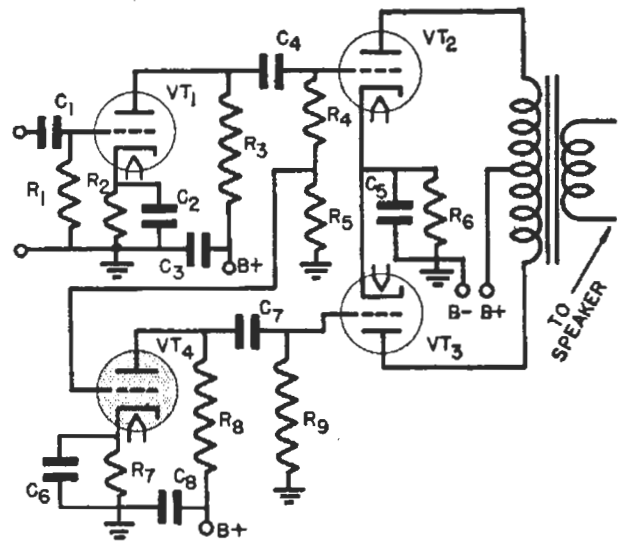


FIG. 34. A basic phase-inverter stage.

vider  $R_4$ - $R_5$  is used to feed a portion of the output voltage from  $VT_1$  to the phase inverter tube  $VT_4$ .

The tube  $VT_4$  amplifies in the normal manner. However, the voltage divider  $R_4$ - $R_5$  is figured out so that if this stage has a gain of, say, 10, then only one-tenth of the voltage across the  $R_4$ - $R_5$  combination is fed to the tube. Hence, there is effectively no gain in the  $VT_4$  stage (10 times 1/10 is 1), and the voltage across  $R_9$  is the same amount as the voltage across  $R_4$ - $R_5$ , so tube  $VT_3$  gets the same amount of signal voltage as does tube  $VT_2$ . (When servicing this type of phase inverter, it is important to replace  $R_4$  and  $R_5$  with

exact duplicate parts when these resistors are found defective. This is necessary so that the proper voltage division will be obtained to counteract the gain of  $VT_4$ .)

What about the phase? When the signal in the grid circuit of  $VT_2$  is going positive, this same signal is fed to the grid of  $VT_4$ . The phase reversal of  $VT_4$  causes the grid of  $VT_3$  to be driven

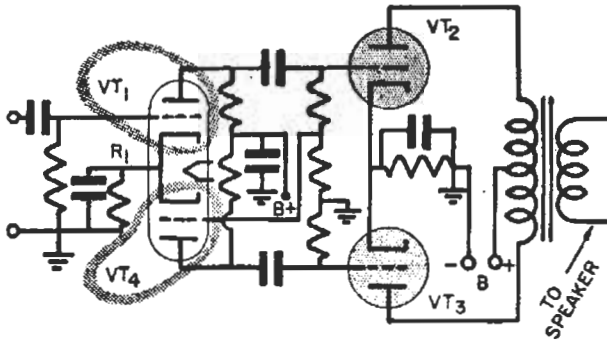


FIG. 35. The phase inverter and the driver are sections of the same dual tube.

negative at this same moment—just what we want to happen.

► Fig. 35 shows another arrangement using the circuit of Fig. 34. Tubes  $VT_1$  and  $VT_4$  are individual sections of a dual-triode tube. The same bias resistor ( $R_1$ ) is used for both sections, a practice that tends to equalize any slight irregularities in the characteristics of  $VT_1$  and  $VT_4$ .

## DEGENERATIVE PHASE INVERTERS

There is danger that aging of the tubes may upset the voltage balance between the outputs of  $VT_1$  and  $VT_4$  even when they are part of the same tube. If an unbalanced voltage is fed into the push-pull circuit, we will get a distorted output, as the even harmonics will not balance out.

One way around this is to use a single tube to feed both the push-pull tubes, as shown in Fig. 36.

First, let's examine the circuit of  $VT_1$ . Tracing the direction of electron

flow from cathode to plate, we find that the end 3 of  $R_4$  is negative with respect to terminal 4. Continuing around through the B supply, and through  $R_3$  back toward the cathode, we find that terminal 2 of  $R_3$  is negative with respect to terminal 1.

Now, let's consider terminal 4 of  $R_4$  to be grounded through  $C_4$  (insofar as a.c. signals are concerned), so that it connects effectively to terminal 2 of  $R_3$ . Comparing the voltages across these two resistors, we find that an increase in plate current makes terminal 3 of  $R_4$  more negative at the same instant that it makes terminal 1 of  $R_3$  more positive. Therefore, if we feed  $VT_2$  from terminal 3 of  $R_4$ , and feed tube  $VT_3$  from terminal 1 of  $R_3$ , the two tubes will be fed out of phase.  $R_3$  and  $R_4$  must be equal in size, of course, so that the voltages fed the push-pull tubes will be equal.

► Since  $R_3$  is part of the plate load, but is also in the input circuit in such

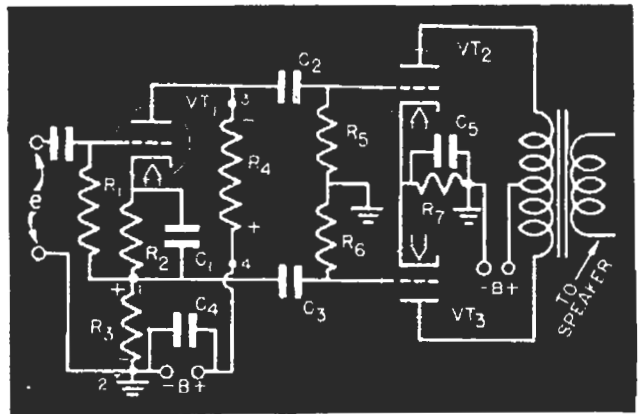


FIG. 36. Both push-pull tubes may be fed from a single tube in this unique phase inverter stage.

a way that the voltage developed across  $R_3$  opposes the input signal voltage, this circuit is degenerative. For example, if the stage gain is 50, then 1 volt across  $R_1$  (the grid resistor) will appear as 25 volts across  $R_4$  and  $R_3$  respectively. (25 plus 25 is 50, the a.c. voltage we would get from a gain of 50.) However, the 25 volts across  $R_3$

must be subtracted from the voltage  $e$  applied at the input terminals, so to get 1 volt across  $R_1$ , we must apply an  $e$  of 26 volts. Hence, the over-all gain of  $VT_1$  is only about 2 ( $50 \div 26$  is about 2). As only half the output voltage is supplied to each of the push-pull tubes, the effective gain is one, so the input voltage  $e$  we supply must be the same as the voltage necessary to drive the grid of one of the push-pull tubes.

As the tube  $VT_1$  ages, the voltage across  $R_3$  and  $R_4$  will tend to decrease, but this lets a slightly increased amount of voltage appear across grid resistor  $R_1$ , and conditions are restored approximately to normal. Furthermore, even if the input voltage increases to large amounts, the resulting increase in voltage across  $R_3$  prevents overload. Thus, all the advantages of degeneration are added to this phase inverter stage.

► The same idea of degeneration is also used in what is called a self-bal-

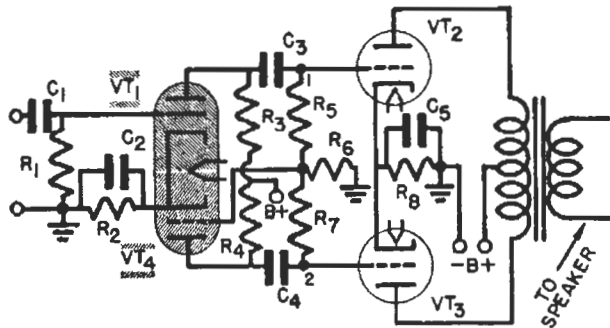


FIG. 37. By making a slight change in the grid feed circuit of the phase inverter stage, a balanced phase inverter, including degeneration, is obtained.

ancing inverter using two tubes. The circuit is shown in Fig. 37. At first glance, it appears to be the same as that of Fig. 35, but notice the position of resistor  $R_6$ . This resistor is placed so that degeneration occurs, and its value is increased to equal that of  $R_5$  (and  $R_7$ ).

Half the voltage between point 1 and ground (point 1 is the grid terminal of  $VT_2$ ) is applied to the grid

of  $VT_4$ . The amplified plate voltage of  $VT_4$  then appears between point 2 and ground; half of it is across  $R_6$ , and is fed back into the grid circuit of  $VT_4$ . Since (as in the circuit of Fig. 36) the output voltage is fed back to the grid of  $VT_4$ , the effective gain is only 2 in-

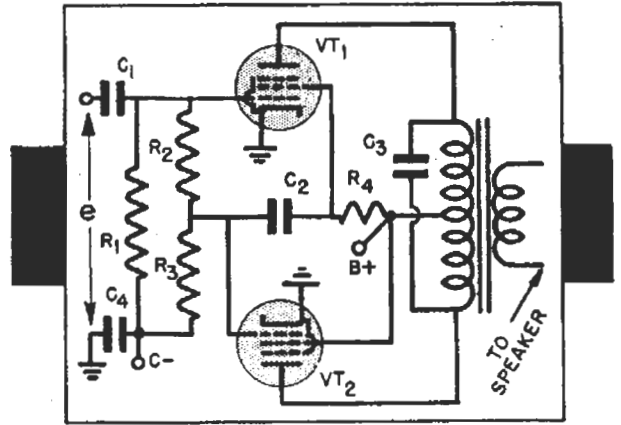


FIG. 38. A special phase inverter circuit used on certain Philco receivers. One of the output tubes is used as the source of the grid voltage for the other.

stead of being the natural gain of the stage (and, since  $VT_4$  gets only half the  $R_5$ - $R_6$  voltage, the gain from point 1 to point 2 is only one—the two voltages are equal). However, this gain is practically independent of the characteristics of tube  $VT_4$ , so the tube can age without upsetting the circuit.

► A somewhat unique phase inverter circuit is shown in Fig. 38. This is used in certain Philco receivers.

Here, the input signal  $e$  is fed directly to the grid of one of the push-pull tubes ( $VT_1$ ) through condenser  $C_1$ . The grid resistor for this tube is  $R_1$ . This tube amplifies the signal in the normal way.

Inserted in the screen grid circuit of tube  $VT_1$  is a small resistor  $R_4$ . This acts as a load resistor, in that a certain amount of the signal energy developed by  $VT_1$  appears across this resistor. In other words, the screen grid acts like a triode plate, and taps off a certain amount of the signal energy, with resistor  $R_4$  acting as its load. The

signal developed across  $R_4$  is fed to the grid of  $VT_2$  through  $C_2$ . Resistor  $R_3$  is the grid resistor for this tube.

Thus, the tube  $VT_1$  serves a dual purpose. It is one of the tubes in the push-pull amplifier, and also acts as the phase inverter for tube  $VT_2$ .

Considerable degeneration is necessary in this circuit to prevent distortion. This is furnished by resistor  $R_2$ , which is a resistance of higher value than either  $R_1$  or  $R_3$ . Through it, some of the energy fed back through  $C_2$  is applied to the grid of  $VT_1$ , opposing the original signal and causing degeneration in this tube. In addition, some

of the input signal  $e$  is fed through  $R_2$  to  $VT_2$  so that it is out of phase with the  $C_2$  voltage. Hence both tubes undergo a certain amount of degeneration. However, degeneration is not carried as far as in the phase inverters we previously described, because nearly normal performance is wanted from  $VT_1$ . Just enough is used to give reasonable fidelity.

► There are a number of other less commonly used phase inverter circuits. However, they all work essentially like the basic ones we have just described, so you will have little trouble in understanding them.

---

## Facts About Low-Frequency Amplifiers

This lesson is an important milestone in your Course. Here, you gain a complete understanding of one of the major kinds of amplifiers. This lesson might also be considered a summary of your previous studies—because you use facts from all the earlier lessons. You put together your knowledge of how condensers and tubes work, facts you have learned about basic amplifiers, your knowledge of sound waves and their characteristics, and your knowledge of the kinds of distortion. So many important facts are in this lesson that you should come back to it from time to time and quickly run through it to refresh your mind on important circuit and stage actions.

► As a summary of the highlights of this lesson, the following facts will be helpful. If any are not clear in your mind, then it is advisable for you to go back over the lesson right now, because you will need these important facts for later lessons.

The low-frequency amplifier deals with the intelligence signal—audio or

video. In sound receivers, the audio signal must be increased in power to operate the reproducer properly, so a power output stage is used. However, power stages require considerable voltage to drive them, so voltage amplifiers are used to increase the output of the demodulator so that it can operate the power output stage properly.

The voltage amplifiers are named according to the devices used to couple the stages together (or to couple to the power output stage). Hence, voltage amplifiers are known as resistance-capacitance-coupled, impedance-coupled, and transformer-coupled stages.

Of these, the resistance-capacitance-coupled stage offers low gain but is capable of the best fidelity characteristics. It is possible to get a frequency range wide enough to make frequency distortion of minor importance. Amplitude distortion can be kept within reasonable limits also, and phase distortion is of importance only in television. (You will learn more about trouble with phase distortion as you study

television receivers in detail.)

When the voltage amplifier has built up the voltage sufficiently, this voltage is used to drive a single-ended or a push-pull power output stage.

► In the single-ended power stage, a single power tube (or tubes in parallel) will be found. The triode offers the best fidelity, but it requires a much higher signal voltage. For this reason, most modern receivers use pentode or beam power tubes. Both the pentode and the beam power tubes have higher power sensitivity than the triode (they require a much smaller grid signal voltage). For example, earlier radio receivers used two or sometimes three voltage-amplifier stages to drive a single triode power output stage. With modern receiver design, a somewhat greater output is obtainable from the demodulator, so it is possible for a single voltage-amplifier stage to give enough voltage to drive pentode or beam power stages.

You may wonder why both pentode and beam power tubes are used when they seem so similar. The beam power tube is somewhat more efficient than the pentode, and does not introduce quite as much third-harmonic distortion because its characteristic curve is shaped in a slightly different way. The pentode tube was introduced first, and is still used for low-power outputs. However, the more efficient beam power tube has replaced the pentode in the majority of receivers.

In power output stages, the high frequencies may be cut down somewhat by the necessity for a by-pass condenser across the plate load, and the low-frequency response depends upon the primary inductance of the output transformer. Even so, it is possible to make the frequency response of these stages fairly good.

However, the pentode and the beam

power tubes introduce considerable *amplitude* distortion. In the single-ended stage, much of the amplitude distortion can be corrected by inverse feedback, and the push-pull output stage has the important advantage of eliminating all even-harmonic distortion that originates in the output stage. Inverse feedback can be used for push-pull stages also, and will cut down the odd-harmonic distortion.

► In order for a push-pull stage to function properly, the grids of the two tubes must be fed  $180^\circ$  out of phase. This requires a special input transformer or a phase inverter tube stage. The input transformer has been practically eliminated from modern receivers because of its undesirable characteristics and rather high cost. Instead, a phase inverter is almost universally used to feed the grid of one of the push-pull tubes.

The two push-pull tubes must be fed with input voltages of the same amplitude. When a phase inverter stage is used, one of the push-pull tubes is fed directly from a voltage amplifier stage. A fraction of the output of this stage is also fed to the phase inverter stage. There this fractional voltage is amplified and inverted in phase; then it is fed to the other push-pull tube. The amplification received in the phase inverter stage is just enough to make the two push-pull grid voltages equal. (A single tube may feed both push-pull tubes if its load is split between its plate and cathode circuits so that phase inversion occurs.)

► Inverse feedback is a system in which part of the output energy is fed back to some point in an amplifier where it will be out of phase. Any distortion or other unwanted component that originates between these points (the output and the point where the feedback is returned) will be fed back

out of phase and thus will tend to cancel itself. Therefore, inverse feedback is particularly used with pentode and beam power tubes to correct their amplitude distortion. Of course, inverse feedback lowers the gain of the stage or stages within the feedback path, so a higher input voltage must be supplied at the input terminals. For this reason, inverse feedback is usually limited to the power output stage and perhaps to one preceding stage. Another voltage amplifying stage must be used ahead of the inverse-feedback circuit to deliver the required input voltage. Naturally, amplitude distortion must be controlled in this voltage amplifier.

The results of inverse feedback are such that a beam power output stage utilizing this circuit can deliver practically the same quality of output as the triode tube and still require somewhat less input voltage than would a triode tube giving the same power output.

► In modern radio receivers, you will recall that there are many kinds of power supplies. Some receivers operate from the power line and use a power transformer. It is almost universal to find a push-pull stage in such sets when they are intended to give good fidelity. On the other hand, if the receiver is an a.c.-d.c. type or is battery operated, there is a limit to the amount of voltage and current available. For this reason, such sets commonly use single-ended power output stages and smaller loudspeakers, which require less power.

In a television set, there may be from one to three voltage-amplifier stages. The television cathode ray tube—the tube on whose face the picture is reproduced—is the “output” stage in a television set. This tube is entirely voltage driven—very little power is needed to modulate the electron stream

within it. Therefore, in a television set, the low frequency (or video) amplifier consists primarily of voltage amplifying stages.

► As a radio serviceman, you are interested in all these stages because the parts are subject to natural breakdowns—condensers open, short-circuit, or change in value; resistors open or burn out; transformers short-circuit and open-circuit; and tubes change their characteristics with age. You need to know just how these amplifiers operate so that you can intelligently choose the proper replacement part.

Of course, when you have the manufacturer's instructions, or the part values are marked, you need only use parts like the originals to get the same results. However, there will be plenty of instances in which you will have to make a replacement and will not know the exact values of parts. Then you can be guided by your knowledge of what will happen if you use a resistor or a condenser that is larger or smaller than the original. Also, your knowledge of how standard circuits work will always be helpful when you meet non-standard circuits.

► You are now in a much better position to judge the fidelity that would be expected from different resistance-coupled amplifiers. However, always remember that some manufacturers make up for the deficiencies of one stage by purposely changing the response of another. Therefore, don't make the mistake of assuming that the response of the amplifier is necessarily poor because the design of one stage happens to sacrifice low frequencies or high frequencies. Another stage may have an excess response to these frequencies, so that the final result of the combination may be a relatively good output.

# Lesson Questions

Be sure to number your Answer Sheet 15FR-2.

Place your Student Number on every Answer Sheet.

Send in your set of answers for this lesson immediately after you finish them, as instructed in the Study Schedule. This will give you the greatest possible benefit from our speedy personal grading service.

1. Does the low-frequency amplifier obtain its input signal directly from: 1, the demodulator; 2, the i.f. amplifier; or 3, the power supply?
2. If the low-frequency response of an R-C coupled amplifier is to be increased, should the capacity of the coupling condenser ( $C_3$  in Fig. 1) be: 1, increased; or 2, decreased?
3. If a stage having a gain of 12 is cascaded with a stage having a gain of 10, what will be the total voltage amplification of the two? 120
4. Will an increase in the ohmic value of the load resistance for a triode tube make the dynamic  $E_G-I_P$  curve for the tube straighter (more linear)? Yes
5. With a triode tube, is the maximum undistorted power obtained when the plate load: 1, is equal to; 2, is one half of; or 3, is twice the plate resistance?
6. What is the purpose of the plate-to-cathode condenser ( $C_3$  in Fig. 14) that is used in power output stages? It prevents oscillation by providing a feedback path.
7. Does the push-pull stage eliminate: 1, even; or 2, odd harmonic distortion?
8. If there is no by-pass condenser across the bias resistor in the cathode circuit, is the inverse feedback: 1, the voltage type; or 2, the current type?
9. What is the purpose of the phase inverter stage? It takes the place of a push-pull transformer by inverting the signal for the 2nd tube.
10. Why is it important to replace resistors  $R_4$  and  $R_5$  in Fig. 34 with exact duplicate parts? To determine the correct voltage to use to counteract the gain in the phase inverter stage.